


# CS429: Computer Organization and Architecture

## Logic Design

Dr. Bill Young  
Department of Computer Science  
University of Texas at Austin

Last updated: February 17, 2020 at 13:55

# Topics of this Slideset

 


To execute a program we need:

- **Communication:** getting data from one place to another
- **Computation:** perform arithmetic or logical operations
- **Memory:** store the program, variables, results

Everything is expressed in terms of bits.

- Communication: Low or high voltage on a wire
- Computation: Compute boolean functions
- Storage: Store bits

# Digital Signals

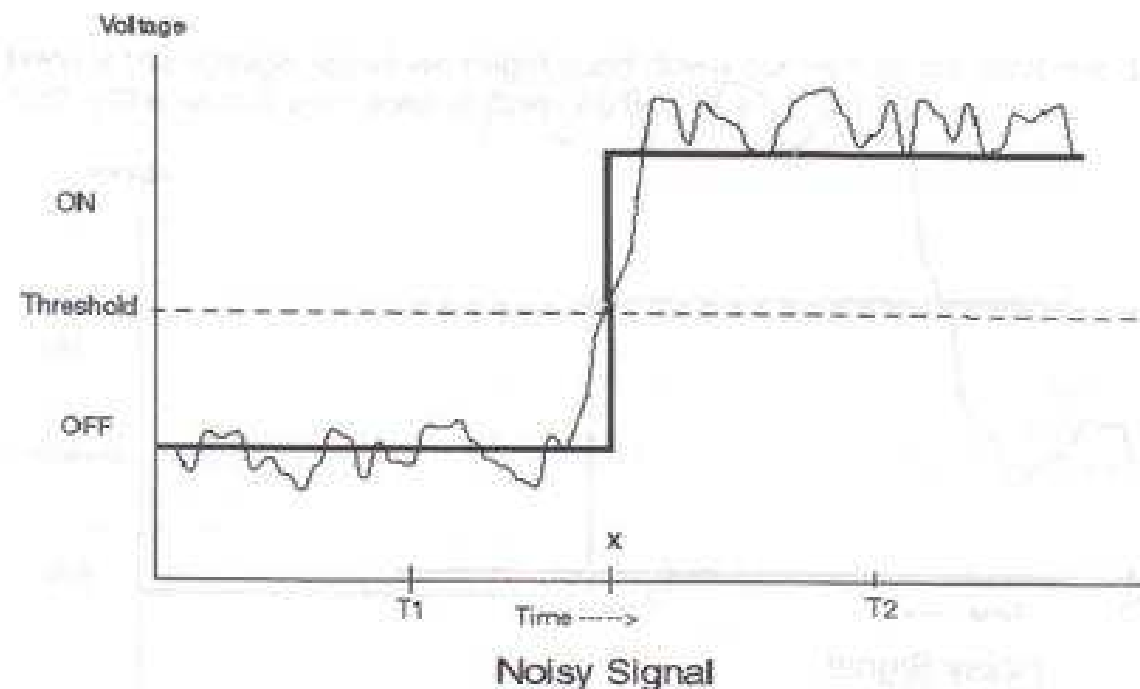

- Use voltage thresholds to extract discrete values from a continuous signal.
- Simplest version: 1-bit signal
  - Either high range (1) or low range (0)
  - With a guard range between them.
- Not strongly affected by noise or low-quality elements; circuits are simple, small and fast.

# Truth Tables

**And:**  $A \& B = 1$  when both  $A = 1$  and  $B = 1$ .

A	B	&
0	0	0
0	1	0
1	0	0
1	1	1

**Or:**  $A | B = 1$  when either  $A = 1$  or  $B = 1$ .

A	B	
0	0	0
0	1	1
1	0	1
1	1	1


**Not:**  $\sim A = 1$  when  $A = 0$ .

A	$\sim$
0	1
1	0


**Xor:**  $A \wedge B = 1$  when either  $A = 1$  or  $B = 1$ , but not both.

A	B	$\wedge$
0	0	0
0	1	1
1	0	1
1	1	0

 What does it mean for a hardware device to represent a boolean function (or truth table), say **and**?



 What does it mean for a hardware device to represent a boolean function (or truth table), say **and**?




- 1 Place on the two input lines voltages representing logical values (T or F).
- 2 After a short *delay*, the output line will stabilize to a voltage representing the logical **and** of the inputs.
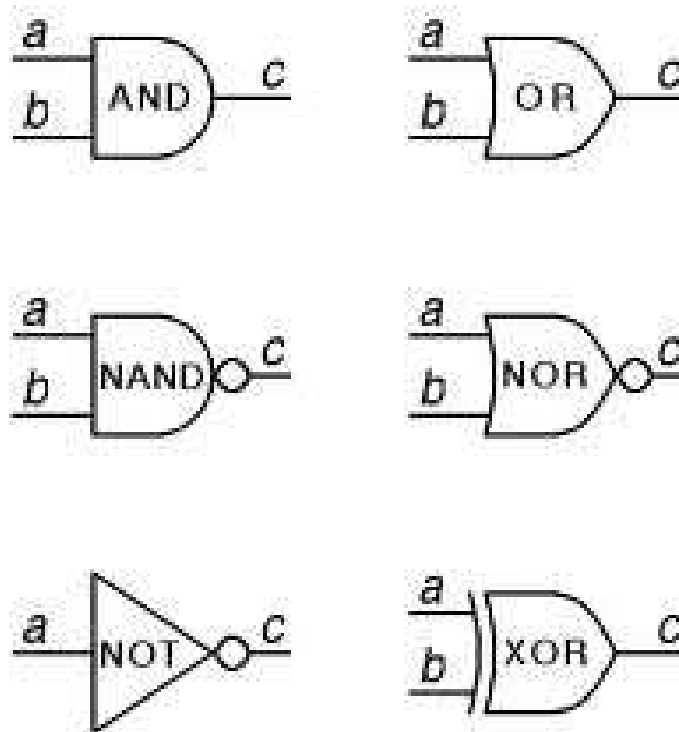
# Computing with Logic Gates

How are these logic functions actually computed in hardware?


- Logic gates are constructed from transistors.
- The output is a boolean function of inputs.
- The gate responds continuously to changes in input *with a small delay*.



How many of these do you really need?
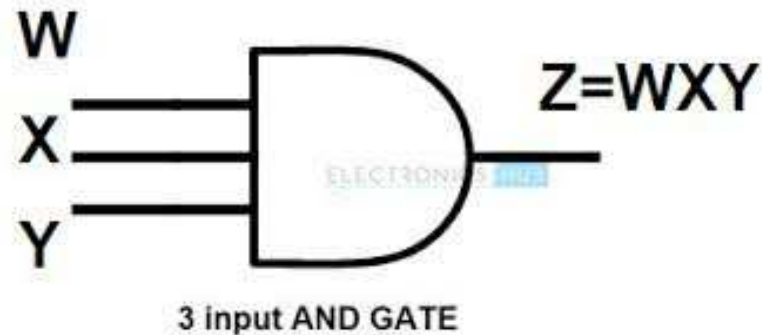
## Aside: Multiple-Input Gates

Some gates allow multiple inputs. For example, a 3-input AND is essentially just a cascade of two 2-input ANDs.






For which gates does it make sense to have extra inputs? For which doesn't it make sense?


   
## Aside: Inverted Inputs/Outputs


A small circle on either the input or output of a gate means that that signal is inverted. That is, it's as if there were an inverter (not) gate there.



What would an **implies** gate look like?
 
# A Complex Function


Primitive boolean functions are implemented by logic gates; more complex functions, by combinations of gates.



A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


$$Z = !A \ || \ (B \ \&\& \ C);$$

# Another Circuit

 

Which wires are connected and which are not? Can you see what this circuit does?

# Another Circuit

 

Which wires are connected and which are not? Can you see what this circuit does?

This is called a *majority circuit*. What function does it compute?

# Sets of Logic Gates

It's pretty easy to see that any boolean function can be implemented with AND, OR and NOT. *Why?* We call that a *functionally complete* set of gates.

You can get by with fewer gates. *How would you show each of the following?*

- AND and NOT is complete.
- OR and NOT is complete.
- NAND is complete.
- NOR is complete.
- AND alone is not complete.
- OR alone is not complete.

Often circuit designers will restrict themselves to a small subset of gates (e.g., just NAND gates). *Why would they do that?*


# Using Logic for Arithmetic

Suppose you wanted to do addition with logic. How might you go about that?
 
# Using Logic for Arithmetic

Suppose you wanted to do addition with logic. How might you go about that?


Define a circuit (full adder) that does one step in an addition:



A	B	Cin	Cout	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

# Full Adder

The following circuit is a full adder:

 


A half adder is a simpler circuit with only inputs A and B.

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




# Adding a Pair of 4-bit Ints

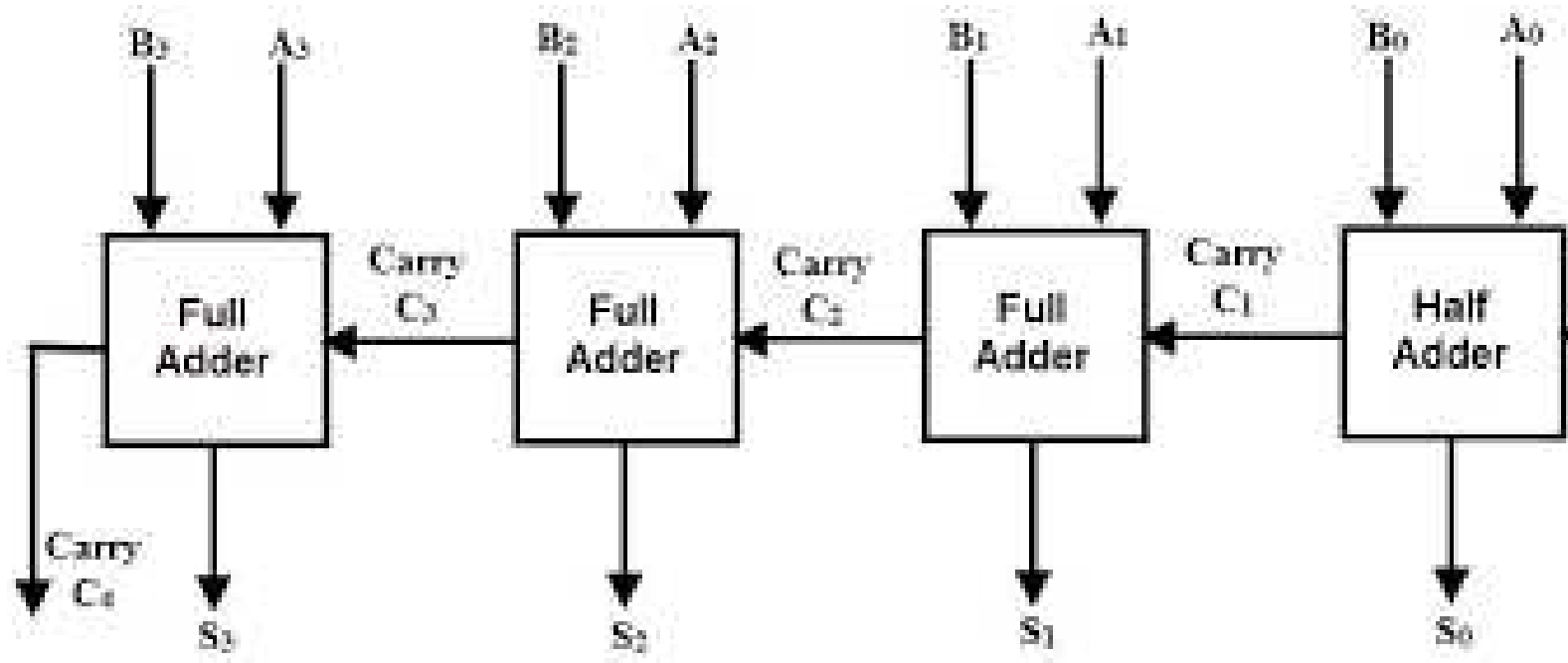

How do you subtract? How do you multiply?

# Combinational Circuits

 


The box contains an acyclic network of logic gates.

- Continuously responds to changes in inputs.
- Outputs become (after a short delay) boolean functions of the inputs.
 
# Bit Equality

The following circuit generates a 1 iff a and b are equal.



```
int eq = (a&&b) || (!a&&!b);
```

Can you design a simpler circuit to do this?

## Hardware description languages (Verilog, VHDL)

- Describe control, data movement, ...
- “Compile” (synthesize) a hardware description into a circuit.

# Verilog Example

One of the more widely used HDL's is Verilog:

```
module simp_circuit (A, B, C, x, y);  
  input A, B, C;  
  output x, y;  
  wire e;  
  and g1 (e, A, B);  
  not g2 (y, C);  
  or g3 (x, e, y);  
endmodule
```

## Hardware Control Language (HCL)

- Very simple hardware description language.
- Boolean operations have syntax similar to C logical operations.
- We'll use it to describe control logic for processors.

## Data types

- `bool`: Boolean ( `a`, `b`, `c`, ... )
- `int`: words ( `A`, `B`, `C`, ... )
- Does not specify word size

## Statements

- `bool a = bool-expr;`
- `int A = int-expr;`


## Boolean expressions

- Logic operations:  $a \ \&\& \ b$ ,  $a \ || \ b$ ,  $!a$
- Word comparisons:  $A \ == \ B$ ,  $A \ != \ B$ ,  $A \ < \ B$ ,  $A \ <= \ B$ ,  
 $A \ >= \ B$ ,  $A \ > \ B$
- Set membership:  $A \ \text{in} \ \{B, C, D\}$


## Word expressions

- Case expressions:  $[a: A; b: B; c: C]$
- Evaluate Boolean expressions  $a$ ,  $b$ ,  $c$  in sequence
- Return corresponding word expression for first successful Boolean evaluation.

# Word Equality

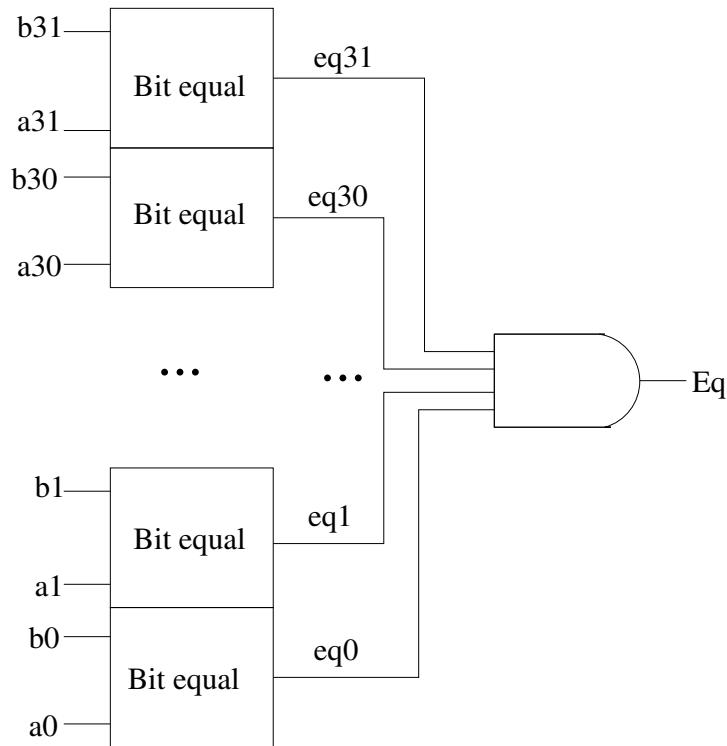

Word-level representation:

 

HCL Representation:


$$Eq = (A == B)$$

Assume 32-bit word size.

HCL representation

- Equality operation
- Generates Boolean value

# Bit Multiplexor

 


HCL Expression:

```
int out = (s && a) || (!s && b);
```


- Control signal  $s$  selects between two inputs  $a$  and  $b$ .
- Output is  $a$  when  $s == 1$ , and  $b$  otherwise.



# Word Multiplexor

 

Word-level representation:

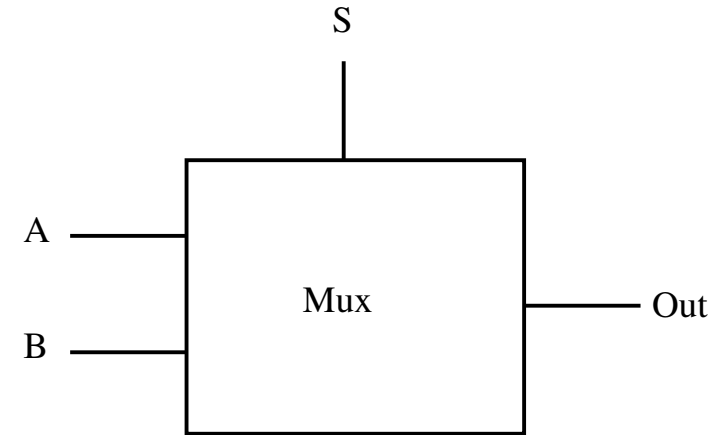


HCL Representation:

```
int Out = [  
    s : A;  
    1 : B;  
];
```

Select input word  $A$  or  $B$  depending on control signal  $S$ .


# Word Examples

Minimum of 3 words

 

```
int Min3 = [  
    A <= B && A <= C : A;  
    B <= A && B <= C : B;  
    1                  : C;  
]
```

4-way Multiplexor

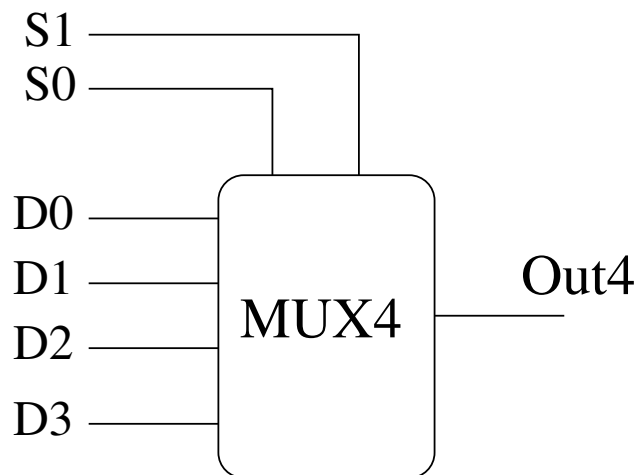


```
int Out4 = [  
    !s1 && !s0 : D0;  
    !s1        : D1;  
    !s0        : D2;  
    1          : D3;  
]
```

What do these do?

## **An ALU is an Arithmetic Logic Unit**

- Multiple functions: add, subtract, and, xor, others
- Combinational logic to perform functions.
- Control signals select function to be performed.
- Modular: multiple instances of 1-bit ALU


# A 4-bit ALU

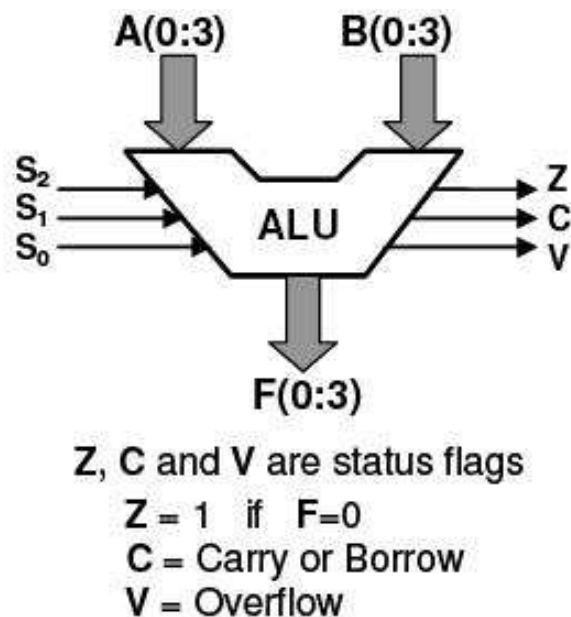

S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Function (F)
0	0	0	A+B
0	0	1	A-B
0	1	0	A-1
0	1	1	A+1
1	0	0	$A \wedge B$
1	0	1	$A \vee B$
1	1	0	NOT A
1	1	1	$A \oplus B$

- Combinational logic: continuously responding to inputs.
- Control signal selects function computed; Y86 ALU has only 4 arithmetic/logical operations.
- Also computes values of condition codes. Note these are not the same as the three Y86 flags:
  - OF: overflow flag
  - ZF: zero flag
  - SF: sign flag

# The Y86 ALU in HCL

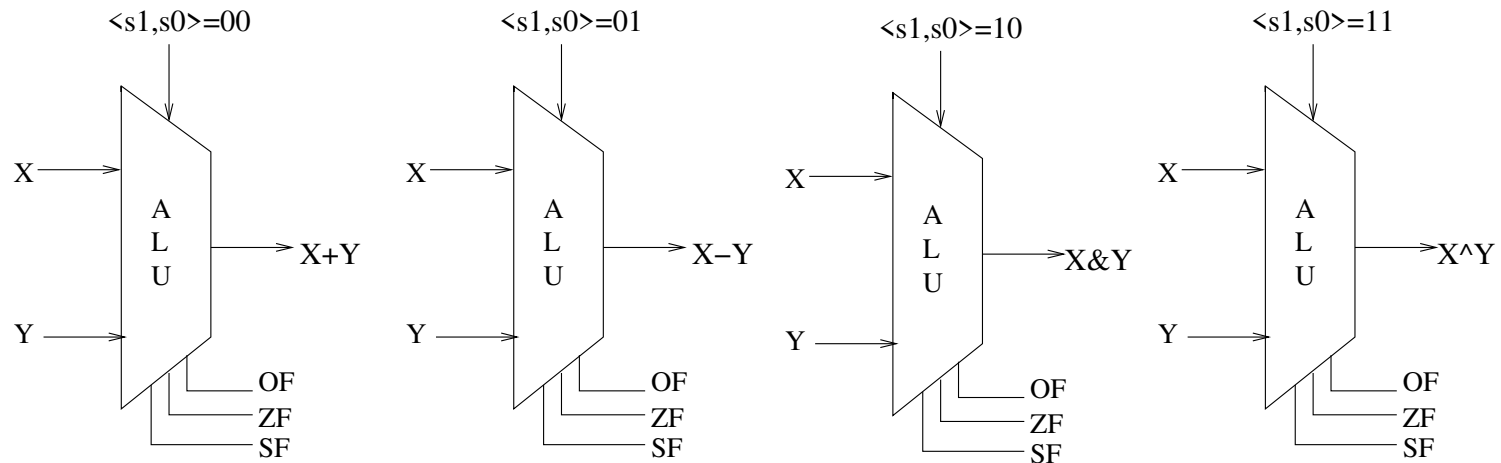

```
int Out = [  
    !s1 && !s0: X+Y;  
    !s1 && s0  : X-Y;  
    s1  && !s0: X&Y;  
    1      : X^Y;  
];
```


# Sequential Logic

How would you design a circuit that records a bit? What does that even mean?
 
# Sequential Logic

How would you design a circuit that records a bit? What does that even mean?

Ideally, you'd like a *bi-stable* device (latch) as follows:



The value on line Q is the current stored value.


Such “state-holding” devices are called *sequential logic* as opposed to *combinational logic*.

To store a new value:

- 1 Line Enable should be low (0).
- 2 Place the bit to store on line Data.
- 3 Raise Enable to high (1).
- 4 The value on line Data is stored in the device.
- 5 Lower Enable to low (0).
- 6 Reading Q returns the stored bit until next store.
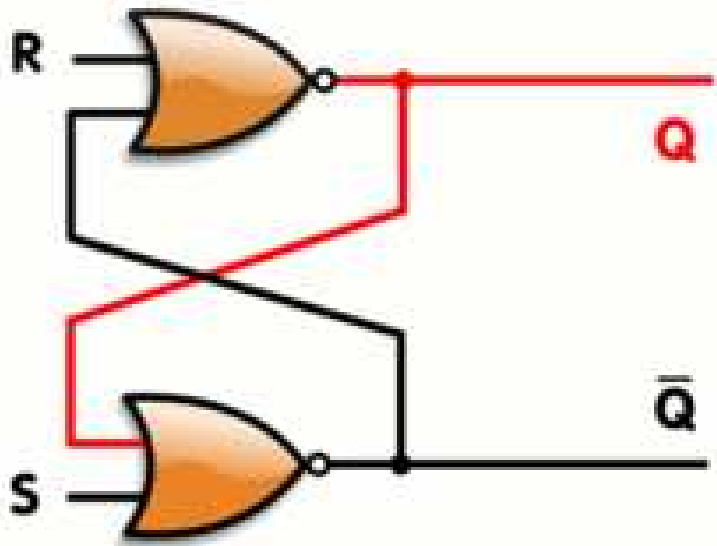
# SR Flip Flop: Storing a Bit

An SR flip flop is a step in the direction of a latch.



Pulse (temporarily raise) the R (reset) input to record a 0.

Pulse the S (set) input to record a 1.


## Characteristic table

S	R	Q <sub>next</sub>	Action
0	0	Q	hold state
0	1	0	reset
1	0	1	set
1	1	X	not allowed


This is not very convenient because it requires pulsing either S or R to record a bit.


 
# Gated D Latch: Store and Access One Bit


 
## Higher level representation D Latch Truth table




E/CP	D	Q	$\bar{Q}$	Comment
0	X	Q	$\bar{Q}$	No change
1	0	0	1	Reset
1	1	1	0	Set

E (enable) and CP (clock pulse) are just two names for the same input.

# A 4-bit Register
 
## 4 D latches:

- All share the E/CP (aka WE or Write Enable) input
- D0–D3 are the data input
- Q0–Q3 are the output




# Register File Abstraction

Register file provides the CPU with temporary, fast storage.

- N registers.
- Each of K bits.
- L output ports.

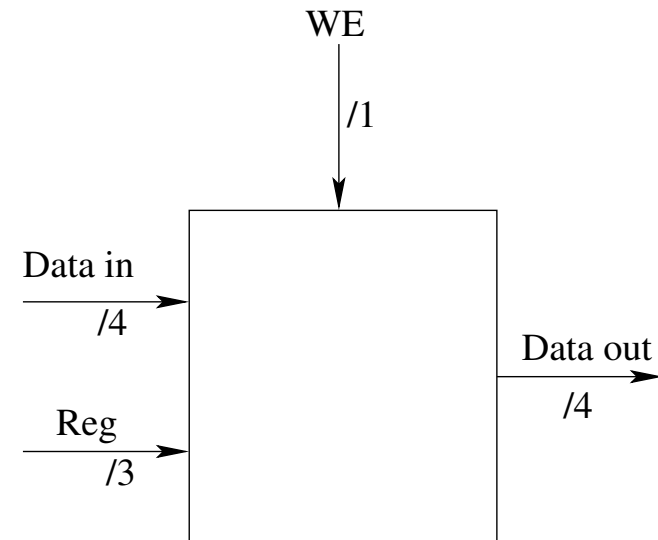
Suppose we want eight 4-bit registers and one output port.


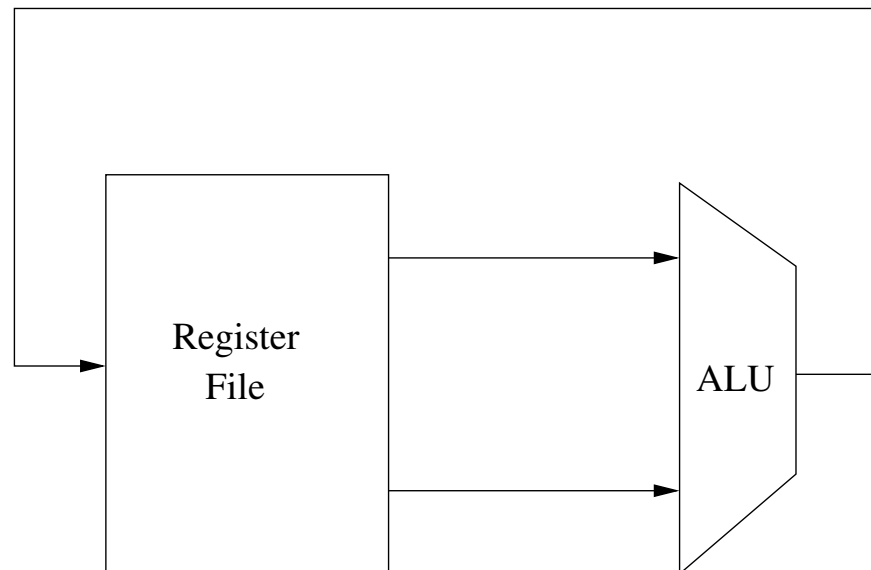
# Race-through Condition with D Latches

Write Enable (WE) must be held at “1” long enough to allow:

- Data to be read;
- Operation (e.g., addition) to be performed;
- Result to be stored in target register.



# Edge Triggered Flip Flops


An edge-triggered flip-flop changes states either at the positive edge (rising edge) or at the negative edge (falling edge) of the clock pulse on the control input.

- A register is made up of several flip flops, each providing storage and access for an individual bit.
- A register file is made up of several registers and control logic
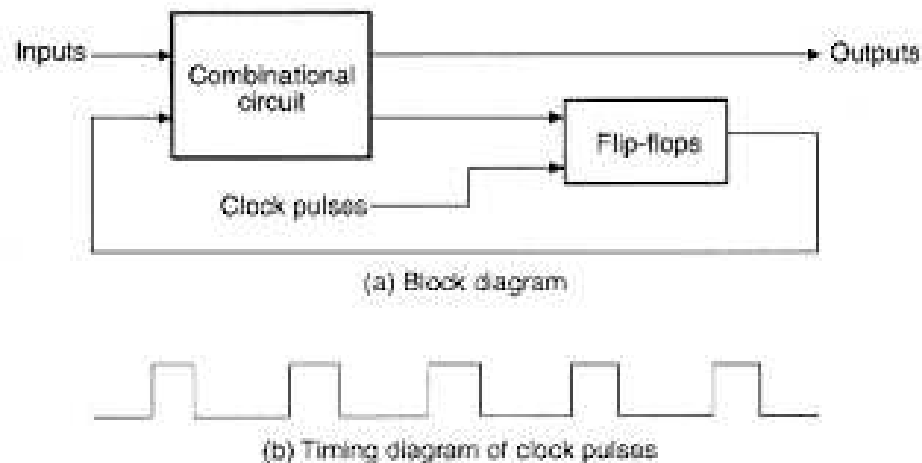
# Clocking

The clock acts to enforce timing control on the chip.

- An integral part of every synchronous system.
- Can be global



Clock Frequency =  $1 / \text{clock period}$

- Measured in cycles per second (Hertz)
- 1 KHz = 1000 cycles / second
- 1ns ( $10^{-9}$  seconds) = 1GHz ( $10^9$ ) clock frequency
- Higher frequency means faster machine speed.

# Random Access Memory (RAM)

## Stores many words

- Conceptually, a large array where each row is uniquely addressable.
- In reality, much more complex to increase throughput.
- Multiple chips and banks, interleaved, with multi-word operations.

## Many implementations

- Dynamic (DRAM) is large, inexpensive, but relatively slow.
  - 1 transistor and 1 capacitor per bit.
  - Reads are destructive.
  - Requires periodic refresh.
  - Access time takes hundreds of CPU cycles.
- Static (SRAM) is fast but expensive.
  - 6 transistors per bit.
  - Streaming orientation.

## Computation

- Performed by combinational logic.
- Implements boolean functions.
- Continuously reacts to inputs.

## Storage

- Registers: part of the CPU.
  - Each holds a single word.
  - Used for temporary results of computation.
  - Loaded on rising clock.
- Memory is much larger.
- Variety of implementation techniques.