




State Machines





Another look at D latch/flip-flop

 

| q_{old} | D | q_{new} |
|-----------|---|-----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

This is an example of a **state diagram**
more specifically a **Moore** machine

$$q_{new} = D$$




Synchronous state machines

If a system can both process and store information, then the values stored in the memory elements depend on both the inputs and the previous values in these elements. This is called a **sequential** system.

Such a system is also called a **finite-state machine (FSM)**.

 If all changes to memory values happen at the same time as determined by a global system clock, we have a **synchronous FSM**.





FSM definition

An FSM has the following components:


- A set of states
- A set of inputs
- A set of outputs
- A state-transition function (of the states and inputs)
- An output function (of the states and maybe inputs)
 - Moore machine - function of states only
 - Mealy machine - function of states and inputs

This can be represented by a **state diagram**

- States are circles
- Arcs show the state transition function
- Arcs are labeled with input values
- Outputs are labels on states (Moore) or arcs (Mealy)



Another example - 2-bit counter

 

Counter starts at 0 (green) and increments each time the clock cycles, until it gets to 3 and then overflows back to 0.

Only input is the clock, we don't show that.

| H_{old} | L_{old} | H_{new} | L_{new} |
|-----------|-----------|-----------|-----------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |





2-bit counter

| H_{old} | L_{old} | H_{new} | L_{new} |
|-----------|-----------|-----------|-----------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |


$$L_{new} = H_{old}'L_{old}' + H_{old}L_{old}' = L_{old}'$$
  
$$H_{new} = H_{old}'L_{old} + H_{old}L_{old}'$$





2-bit counter with reset

 


| R | H _{old} | L _{old} | H _{new} | L _{new} |
|---|------------------|------------------|------------------|------------------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | x | x | 0 | 0 |

$$\begin{aligned}
 L_{\text{new}} &= R'H_{\text{old}}'L_{\text{old}}' + R'H_{\text{old}}L_{\text{old}}' \\
 &= R'L_{\text{old}}' = (R + L_{\text{old}})'
 \end{aligned}$$

$$\begin{aligned}
 H_{\text{new}} &= R'H_{\text{old}}'L_{\text{old}} + R'H_{\text{old}}L_{\text{old}}' \\
 &= R'(H_{\text{old}}'L_{\text{old}} + H_{\text{old}}L_{\text{old}}')
 \end{aligned}$$



2-bit counter with reset


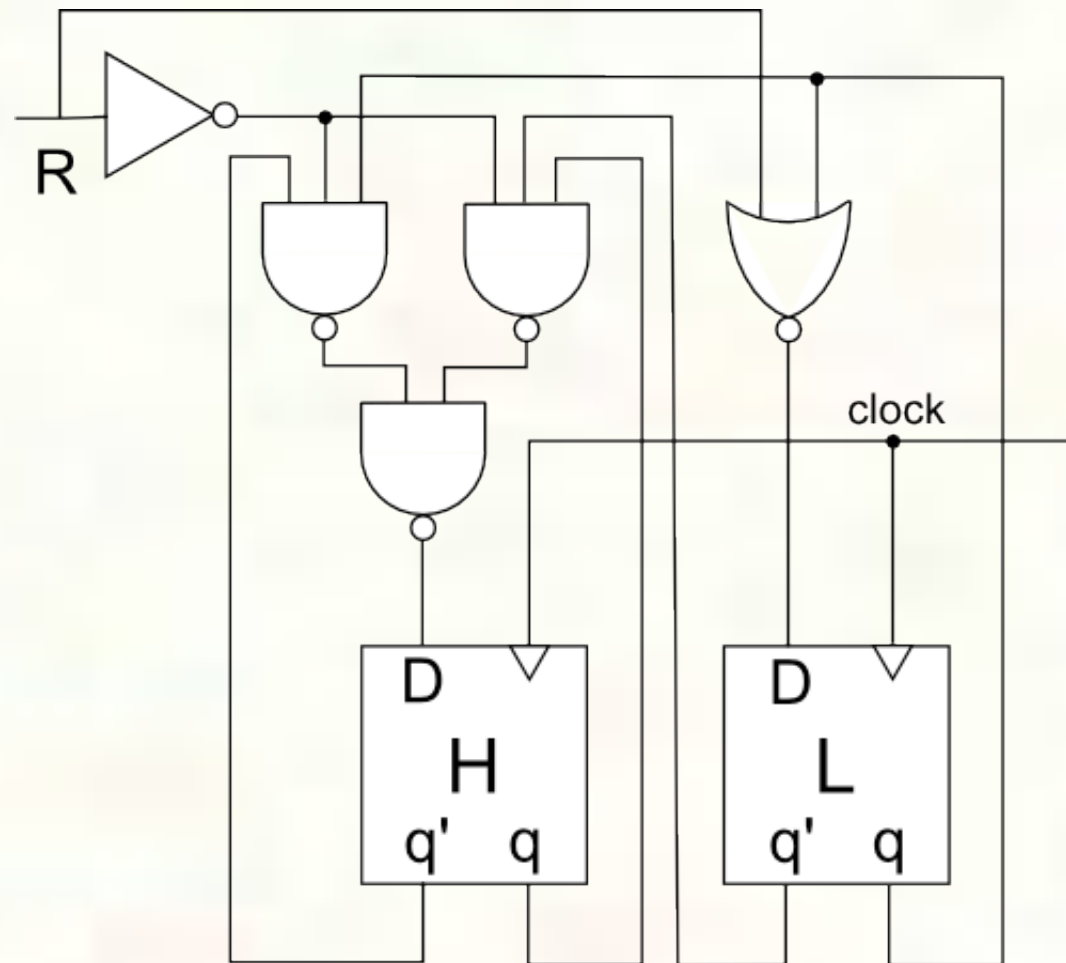




Counter with 7-segment display

Each segment in the display can be lit independently to allow all 10 decimal digits to be displayed (also hex)

  2-bit counter will need to display digits 0-3, so will output a 1 for each segment to be lit for a given state





Counter with output functions

| R | H ₀ | L ₀ | H _n | L _n | A | B | C | D | E | F | G |
|---|----------------|----------------|----------------|----------------|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | X | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

$$A = D = R'H_0'L_0' + R'H_0L_0' + R'H_0L_0 = R'(H_0'L_0)'$$

$$B = R'$$

$$C = R'(H_0L_0)'$$


$$E = R'L_0'$$

$$F = R'H_0'L_0' = (R+H_0+L_0)'$$

$$G = R'H_0$$




7-segment output logic

 



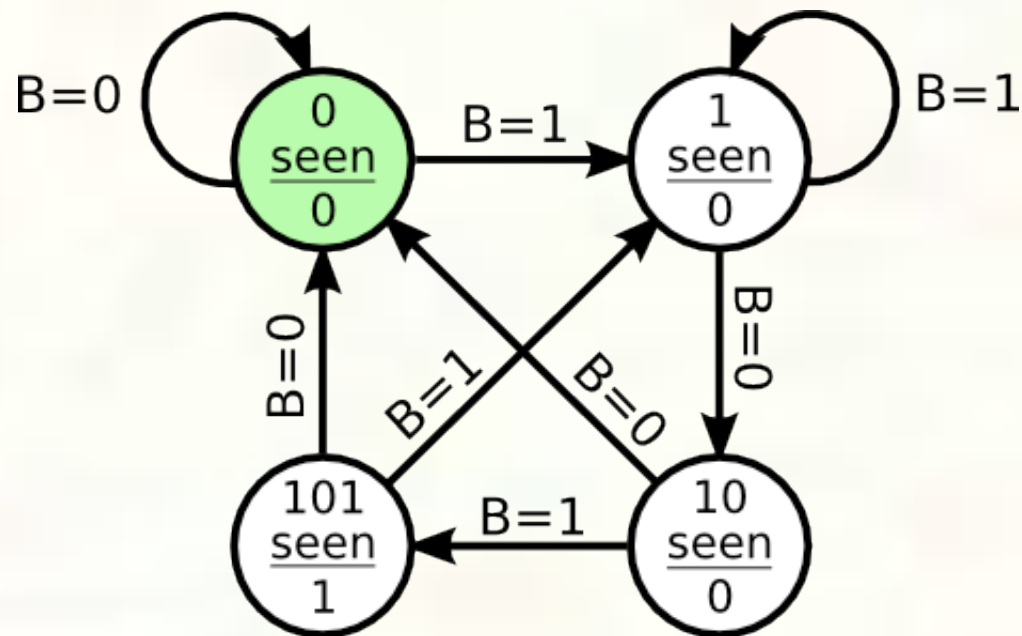Example - 101 lock

Combination lock with 101
being the combination



B is input signal to the lock,
X is output signal to unlock

| B | H ₀ | L ₀ | H _n | L _n | X |
|---|----------------|----------------|----------------|----------------|---|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 |



101 combination lock

$$X = H_0 L_0$$

$$H_n = B'H_0'L_0 + BH_0L_0'$$

$$\begin{aligned} L_n &= BH_0'L_0 + BH_0L_0' + BH_0L_0 \\ &= BH_0'L_0 + BH_0L_0 + BH_0L_0' + BH_0L_0 \\ &= BL_0 + BH_0 \end{aligned}$$



LC-3 datapath

