
Verilog for Control Logic

Paul Gratz

Outline

- Control Logic Modeling Methods
 - Non Procedural
 - Continuous assignments
 - Procedural
 - Always blocks
 - Conditional statements
 - Multi-way Branch (Case)- statements
 - Loops
 - State Machine example
- Synthesis to Structural Verilog

Non-Procedural Control logic

```
assign    head_plus = in_array_addr + 1;
assign    tail_plus = out_array_addr + 1;
assign    tail_plus2 = out_array_addr + 2;
assign    saq_wr_clk = ~clk & saq_we;
```

- Simple
- Explicit
- Difficult to express complicated expressions
- State must be saved for sequential logic


Procedural Control Logic

- Often easier to code.
- Can handle state without having to specify sequential cells.
- Is non-implementation specific.
- Potentially dangerous from the point of view of creating real hardware. Must pay attention to buildability of the design.

Always blocks revisited

```
input  signal1, signal2, signal3;
output output1, output2;
reg    output1, output2;

always @ (signal1 or signal2 or signal3) begin
    output1 = signal1 | ~signal2;
    output2 = signal2 & ~signal3;
end
```

 

- Whenever any “signalX” changes the two outputs are recalculated.
- Easily done in an assignment statement as well.
- Must make sure all signals tested are listed in “@ ()” condition.
- This is non-sequential as shown

Conditional Statements

```
always @ (signal1 or signal2 or signal3) begin
    if (signal1 | ~signal2)
        output1 = 1'b1;
    else
        output1 = 1'b0;
    if (signal2 & ~signal3)
        output2 = 1'b1;
    else
        output2 = 1'b0;
end
```

- Equivalent to the last slide but uses if statements.
- Must be sure to always include “else” for each conditional or will cause instantiation of latches (unless you want latches...).

Multi-way Branching


```
always @ ( signal1 or signal2) begin
    case ({signal1,signal2})          // Case for "or" part of logic block
        2'b00:
            output1 = 1'b1;
        2'b01:
            output1 = 1'b0;
        2'b10:
            output1 = 1'b1;
        2'b11:
            output1 = 1'b1;
        default:
            output1 = 1'b0;
    endcase // case({signal1,signal2})
end
```

- Always (always, always!) use a default statement unless you mean to instantiate a latch (usually you do not).
- Case statements are great for specifying state machines.

Loops

- Don't use them outside of testbenches!
- They are not synthesizable (mostly).
- Have little relation to hardware (usually).
- Generally a bad idea unless you are sure you know what you are doing.

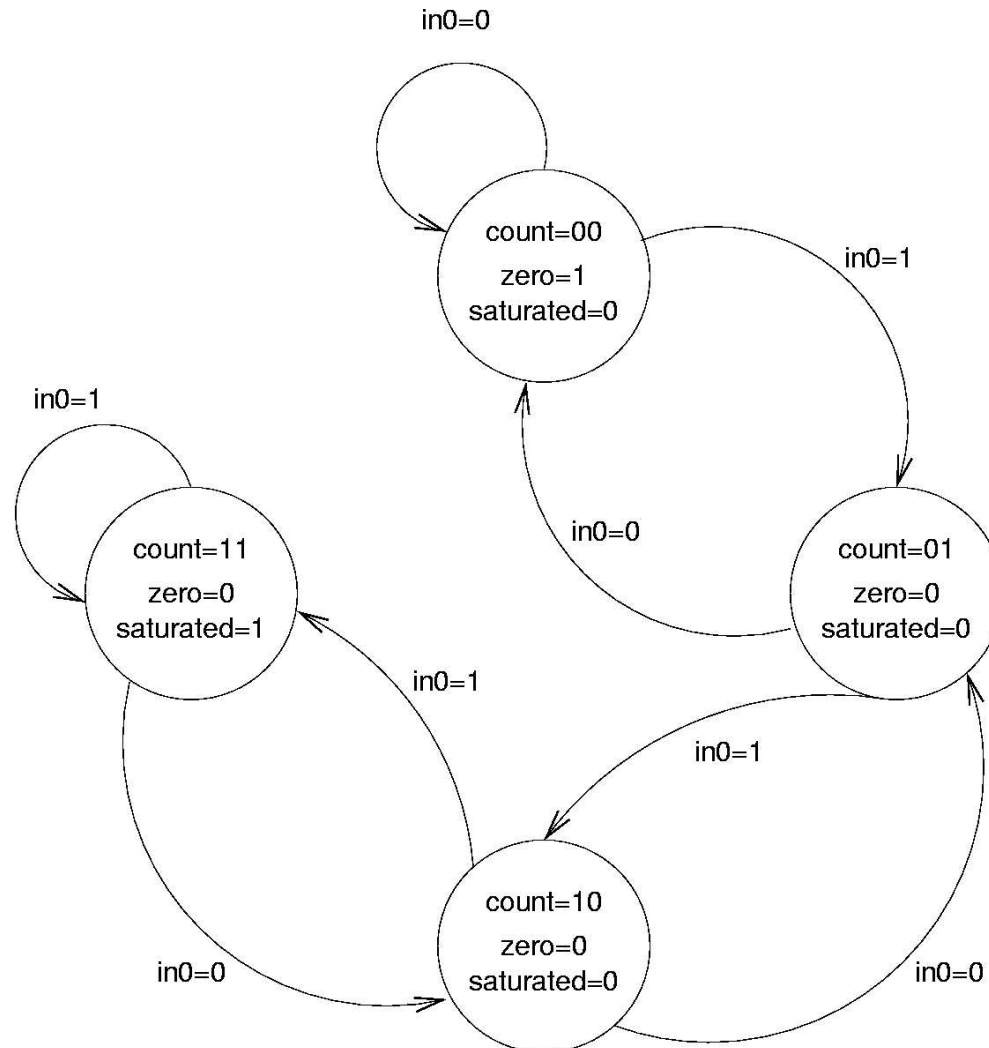State Machine Example: Saturating Counter



State Machine Example: Continued

```
module always_test (/*AUTOARG*/
    // Outputs
    count, zero, saturated,
    // Inputs
    in0, clk, reset
) ;

input in0, clk, reset;
output [1:0] count;
output zero, saturated;
reg [1:0] count, next_count;
reg zero, saturated;

always @ ( /*AUTONSENSE*/count or in0) begin
    case (count)
        2'b00: begin
            zero = 1'b1;
            saturated = 1'b0;
            if (in0)
                next_count = 2'b01;
            else
                next_count = 2'b00;
        end
        2'b01: begin
            zero = 1'b0;
            saturated = 1'b0;
            if (in0)
                next_count = 2'b10;
            else
                next_count = 2'b00;
        end
        2'b10: begin
            zero = 1'b0;
            saturated = 1'b0;
            if (in0)
                next_count = 2'b11;
            else
                next_count = 2'b01;
        end
        default: begin // also could have used "2'b11:" here
            zero = 1'b0;
            saturated = 1'b1;
            if (in0)
                next_count = 2'b11;
            else
                next_count = 2'b10;
        end
    endcase // case(count)
end

always @(posedge clk) begin
    if (reset)
        count = 2'b00;
    else
        count = next_count;
end
endmodule // always_test
```

Synthesis

- Automated process.
- Used to make behavioral style verilog into structural instantiations of library cells.
- Give the tool design constraints and it will try to produce logic that fits them.
- Have to be careful to make sure the logic you intend is what you get.
- The only purpose of behavioral verilog is to be synthesized into real logic.