



Intro to Verilog


A quick tutorial introduction to verilog



Outline


- ◆ Logic Overview
 - Logic Networks
- ◆ Verilog
 - Structural Verilog
 - Description
 - Example
 - Behavioral Verilog
 - Description
 - Example
 - Testing

Basic Logic Network

 

$$\text{Out} = A*B*C + (DE)' + F$$

Network Subdivision

 

$$X = A*B*C \quad Y = (D*E)' \quad \text{Out} = X + Y + F$$

Verilog


- ◆ Unlike other programming languages, verilog is a formalized description of hardware.
- ◆ Verilog statements are concurrent (unless otherwise noted)
- ◆ Two types of verilog:
 - Structural: Allows interconnection of pre-built blocks.
 - Behavioral: Allows use of high level constructs to describe function of hardware w/o having to describe the details.

Structural Verilog

- ◆ Defines the interconnections between blocks.
- ◆ Can be thought of as a “Text Schematic Diagram”

Structural Verilog Example

Schematic:

 


Structural Verilog:

```
module func_x ( X, A, B, C ) ;
    output X;
    input A, B, C;
    and3 my_and3 ( .out(X), .in0(A), .in1(B), .in2(C));
endmodule
```

Structural Verilog Example Cont.

Schematic:

 


Structural Verilog:

```
module func_y ( Y, D, E ) ;
    output Y;
    input D, E;
    wire conn;
    and2 my_and2 ( .out(conn), .in0(D), .in1(E));
    inv my_inv ( .out(Y), .in(conn));
endmodule
```

Structural Verilog Example Cont.

Schematic:

 


Structural Verilog:

```
module func_out ( OUT, X, Y, F ) ;
    output OUT;
    input X, Y, F;
    or3 my_or3 ( .out(OUT), .in0(X), .in1(Y), .in2(F));
endmodule
```

Structural Verilog Example Cont.

Schematic:

 

Structural Verilog:

```
module top ( OUT, A, B, C, D, E, F ) ;
    output OUT;
    input A, B, C, D, E, F;
    wire X, Y;
    func_x my_x ( .X(X), .A(A), .B(B), .C(C));
    func_y my_y ( .Y(Y), .D(D), .E(E));
    func_out my_out ( .OUT(OUT), .X(X), .Y(Y), .F(F));
endmodule // top
```

Behavioral Verilog

- ◆ Allows the designer to specify the function of the device being designed.
- ◆ Designer works at a higher abstraction level.
- ◆ Synthesis tools produce structural verilog from this.

Behavioral Verilog Example


Three Input And Gate:

```
module and3 ( out, in0, in1, in2 ) ;  
    output out;  
    input  in0, in1, in2;  
    assign out = in0 & in1 & in2;  
endmodule // and3
```

(p92 in Palnitkar for other operators)

Behavioral Verilog Example Cont.

Schematic:

 

Behavioral Verilog:

```
module top_2 ( OUT, A, B, C, D, E, F ) ;
    output OUT;
    input  A, B, C, D, E, F;

    assign OUT = (A & B & C) | (~(D & E)) | F;
endmodule
```

Testing

- ◆ Create a verilog file that wraps around the top level of your design called a “testbench” or “stim file”.
- ◆ Provides inputs to your design that change with time.
- ◆ Checks that the output’s are correct for those inputs at any given time.
- ◆ You will be provided with a test bench for the first couple assignments.