


# Systems I

## Datapath Design III

### Topics

- Control logic for instruction execution
- Timing and clocking


# Fetch Logic

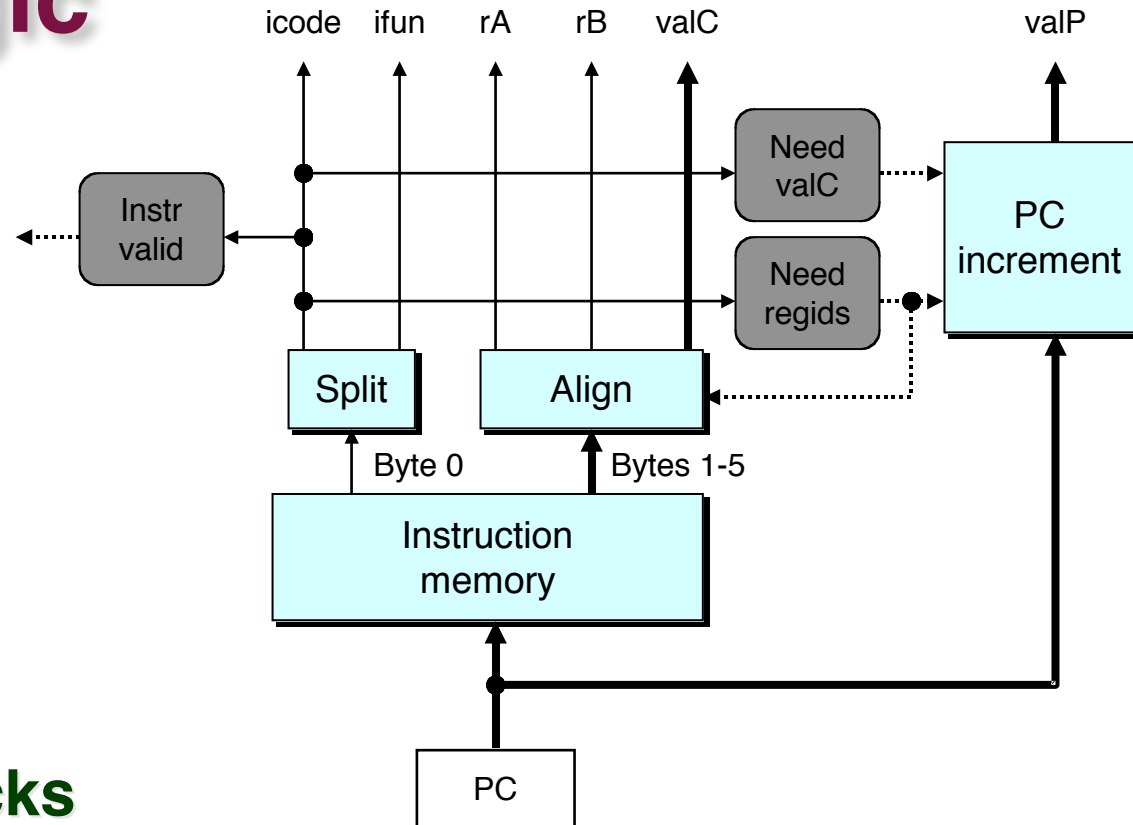

## Predefined Blocks

- **PC:** Register containing PC
- **Instruction memory:** Read 6 bytes (PC to PC+5)
- **Split:** Divide instruction byte into icode and ifun
- **Align:** Get fields for rA, rB, and valC


# Fetch Logic

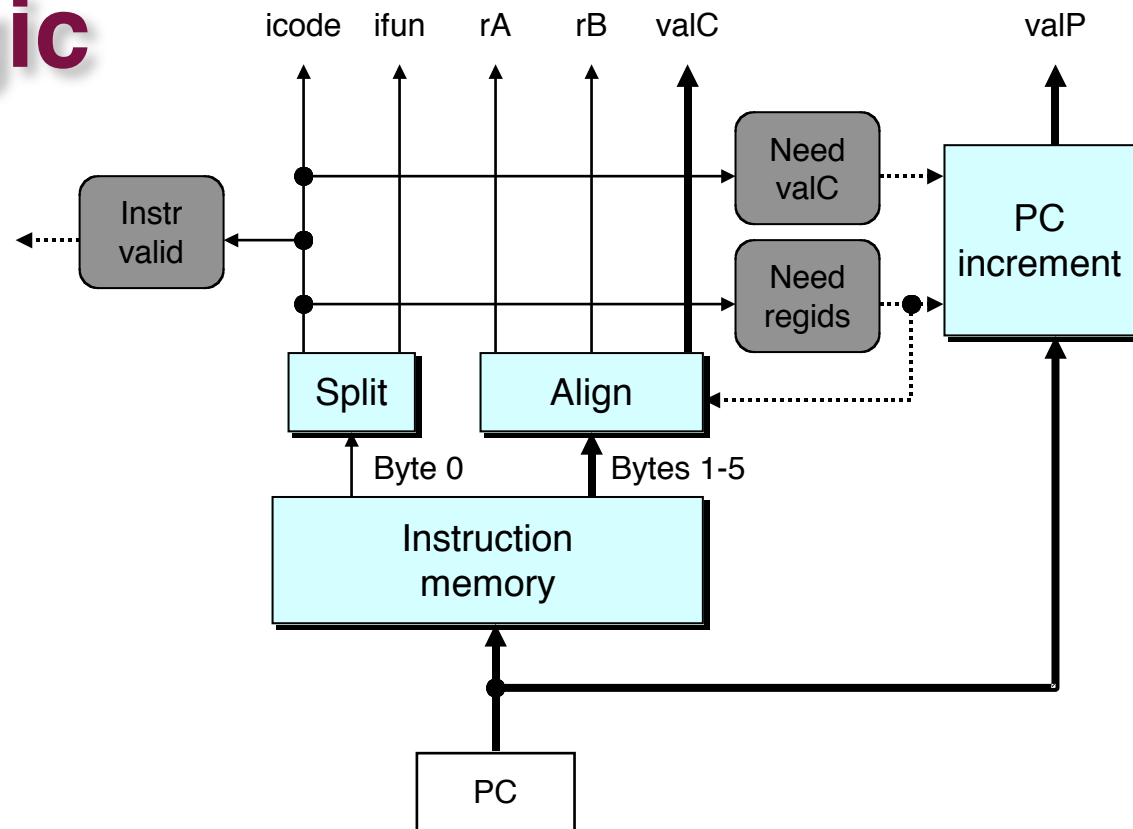

## Control Logic

- **Instr. Valid:** Is this instruction valid?
- **Need regids:** Does this instruction have a register bytes?
- **Need valC:** Does this instruction have a constant word?

# Fetch Control Logic

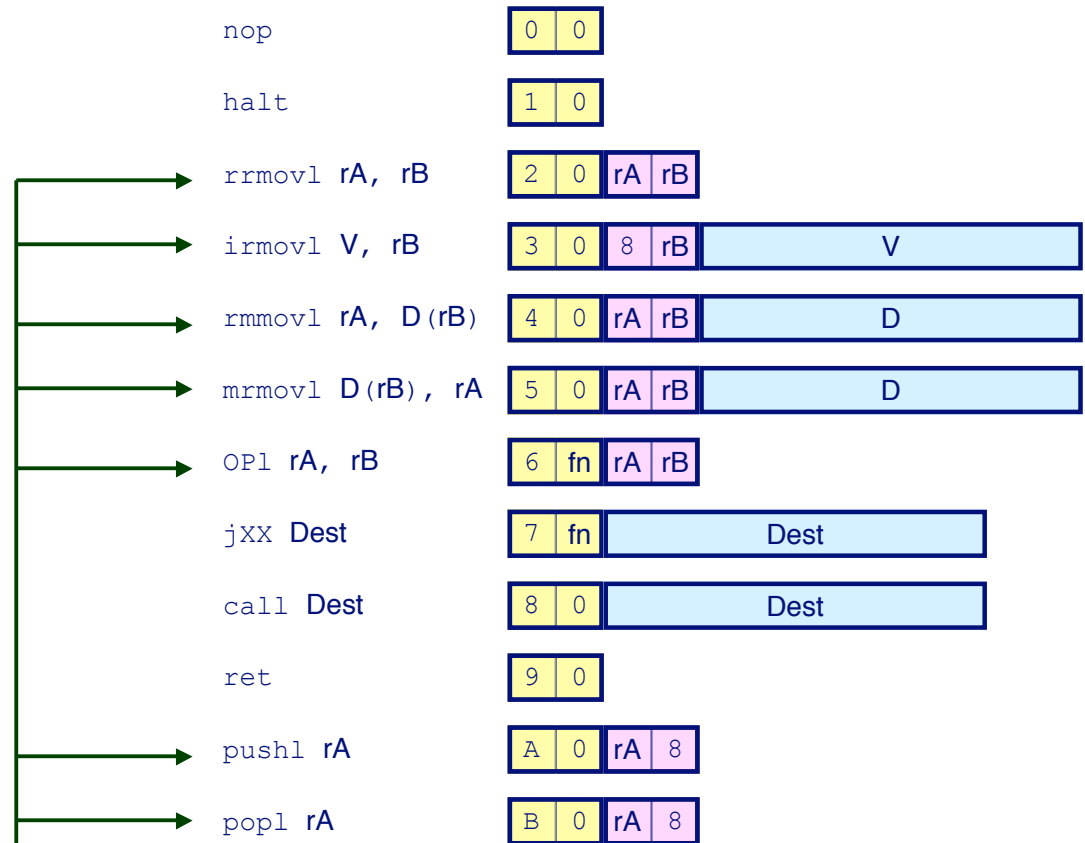

```
bool need_regids =
    icode in { IRRMOVL, IOPL, IPUSHL, IPOPL,
              IIRMOVL, IRMMOVL, IMRMOVL };
```

```
bool instr_valid = icode in
    { INOP, IHALT, IRRMOVL, IIRMOVL, IRMMOVL, IMRMOVL,
      IOPL, IJXX, ICALL, IRET, IPUSHL, IPOPL };
```


# Decode Logic

## Register File

- Read ports A, B
- Write ports E, M
- Addresses are register IDs or 8 (no access)
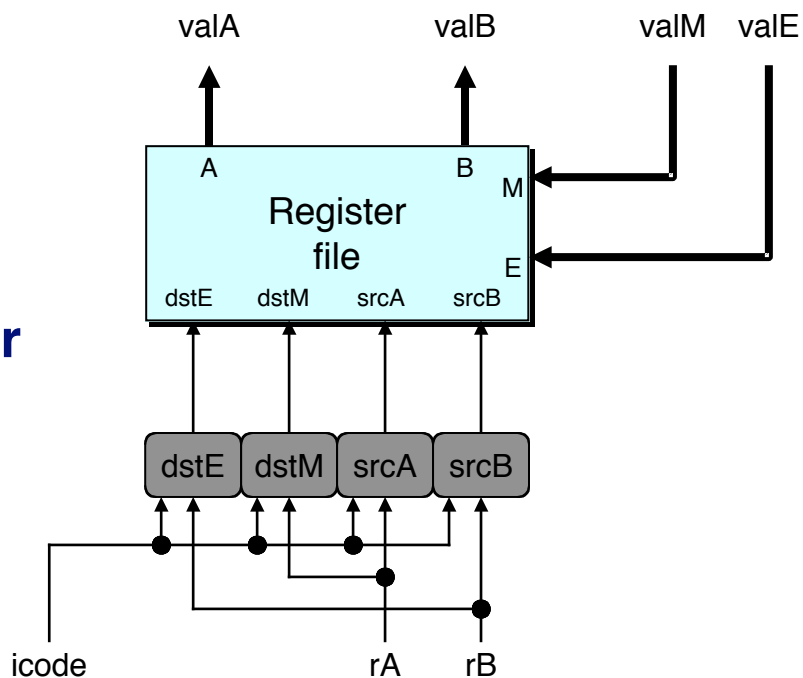
## Control Logic

- srcA, srcB: read port addresses
- dstA, dstB: write port addresses



# A Source

	OPl rA, rB	
Decode	valA ← R[rA]	Read operand A
	rmmovl rA, D(rB)	
Decode	valA ← R[rA]	Read operand A
	popl rA	
Decode	valA ← R[%esp]	Read stack pointer
	jXX Dest	
Decode		No operand
	call Dest	
Decode		No operand
	ret	
Decode	valA ← R[%esp]	Read stack pointer

```
int srcA = [
    icode in { IRRMOVL, IRMMOVL, IOPL, IPUSHL } : rA;
    icode in { IPOPL, IRET } : RESP;
    1 : RNONE; # Don't need register
];
```

# E Destination

	OPl rA, rB	
Write-back	R[rB] ← valE	Write back result
	rmmovl rA, D(rB)	
Write-back		None
	popl rA	
Write-back	R[%esp] ← valE	Update stack pointer
	jXX Dest	
Write-back		None
	call Dest	
Write-back	R[%esp] ← valE	Update stack pointer
	ret	
Write-back	R[%esp] ← valE	Update stack pointer

```
int dstE = [
    icode in { IRRMOVL, IIRMOVL, IOPL } : rB;
    icode in { IPUSHL, IPOPL, ICALL, IRET } : RESP;
    1 : RNONE; # Don't need register
];
```


# Execute Logic

## Units

- **ALU**
  - Implements 4 required functions
  - Generates condition code values
- **CC**
  - Register with 3 condition code bits
- **bcond**
  - Computes branch flag
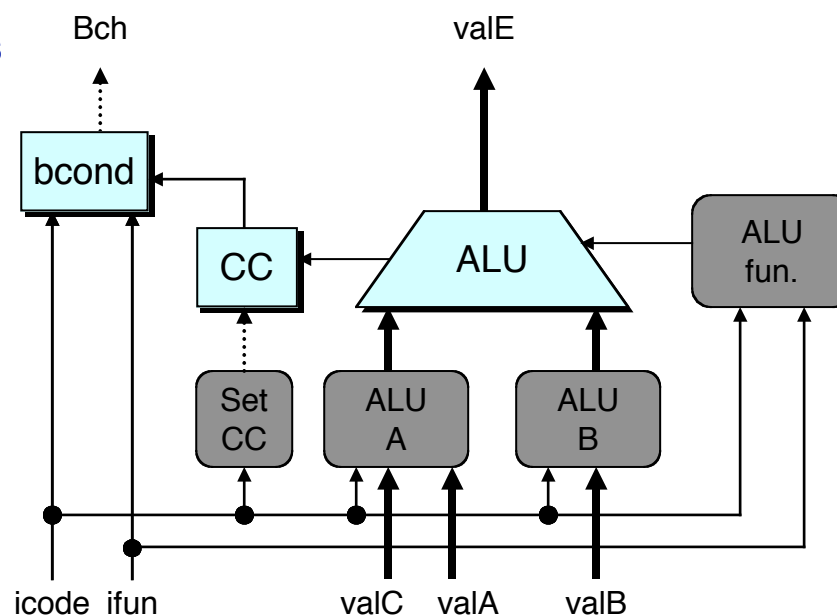
## Control Logic

- **Set CC:** Should condition code register be loaded?
- **ALU A:** Input A to ALU
- **ALU B:** Input B to ALU
- **ALU fun.:** What function should ALU compute?





# ALU A Input

	OPl rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popl rA	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer

```
int aluA = [  
    icode in { IRRMOVL, IOPL } : valA;  
    icode in { IIRMOVL, IRMMOVL, IMRMOVL } : valC;  
    icode in { ICALL, IPUSHL } : -4;  
    icode in { IRET, IPOPL } : 4;  
    # Other instructions don't need ALU  
];
```

# ALU Operation

	OPl rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popl rA	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer

```
int alufun = [  
    icode == IOPL : ifun;  
    1 : ALUADD;  
];
```


# Memory Logic

## Memory

- Reads or writes memory word
 
## Control Logic

- Mem. read: should word be read?
- Mem. write: should word be written?
- Mem. addr.: Select address
- Mem. data.: Select data



# Memory Address

	OPl rA, rB	
Memory		No operation
	rmmovl rA, D(rB)	
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
	popl rA	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	$M_4[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
	ret	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address

```
int mem_addr = [
    icode in { IRMMOVL, IPUSHL, ICALL, IMRMOVL } : valE;
    icode in { IPOPL, IRET } : valA;
    # Other instructions don't need address
];
```

# Memory Read


	OPl rA, rB	
Memory		No operation
	rmmovl rA, D(rB)	
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
	popl rA	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	$M_4[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
	ret	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address

```
bool mem_read = icode in { IMRMOVL, IPOPL, IRET };
```

# PC Update Logic

## New PC

- Select next value of PC

 


# PC Update

	OPl rA, rB	
PC update	PC ← valP	Update PC
	rmmovl rA, D(rB)	
PC update	PC ← valP	Update PC
	popl rA	
PC update	PC ← valP	Update PC
	jXX Dest	
PC update	PC ← Bch ? valC : valP	Update PC
	call Dest	
PC update	PC ← valC	Set PC to destination
	ret	
PC update	PC ← valM	Set PC to return address

```
int new_pc = [  
    icode == ICALL : valC;  
    icode == IJXX && Bch : valC;  
    icode == IRET : valM;  
    1 : valP;  
];
```

# SEQ Operation

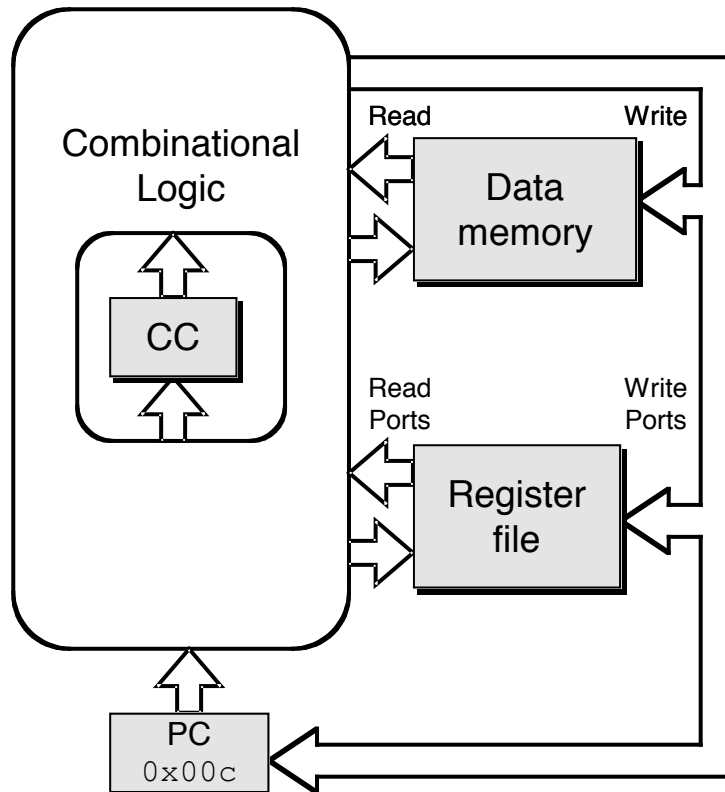

## State

- PC register
- Cond. Code register
- Data memory
- Register file



*All updated as clock rises*

## Combinational Logic

- ALU
- Control logic
- Memory reads
  - Instruction memory
  - Register file
  - Data memory





# SEQ Operation #2

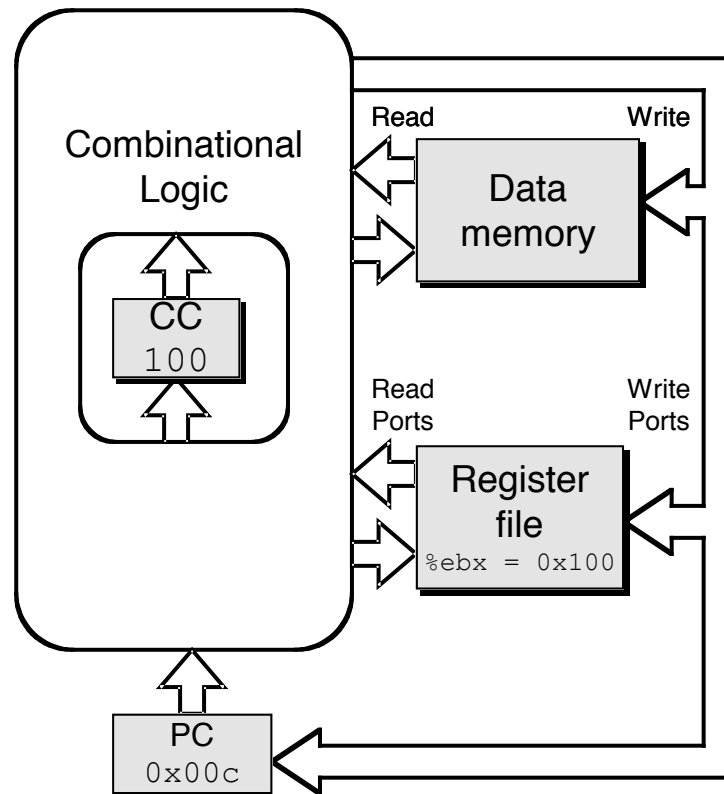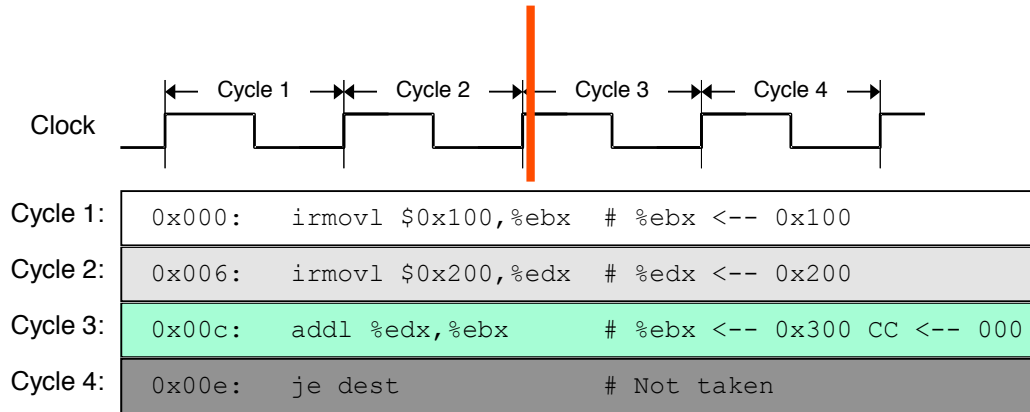



- state set according to second `irmovl` instruction
- combinational logic starting to react to state changes

# SEQ Operation #3

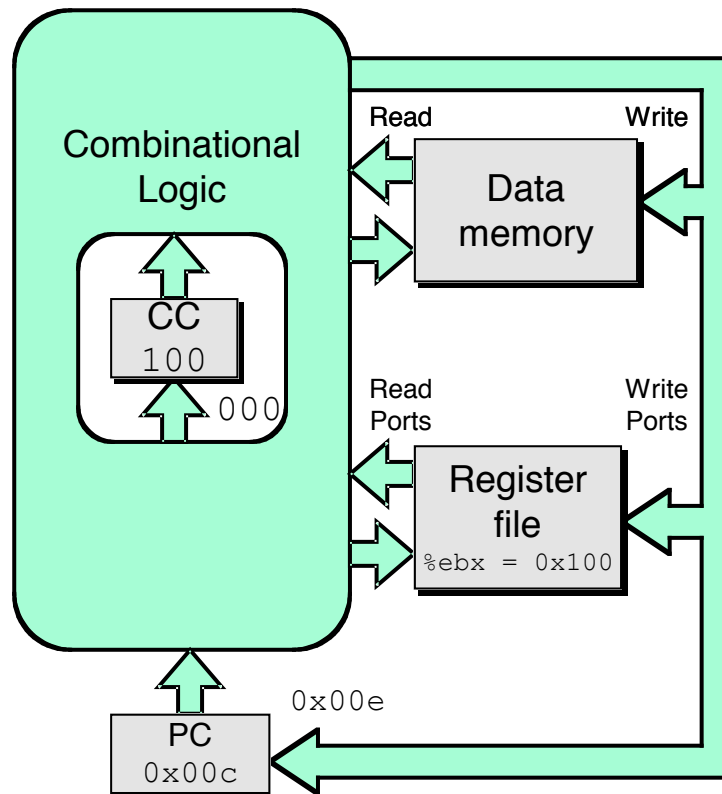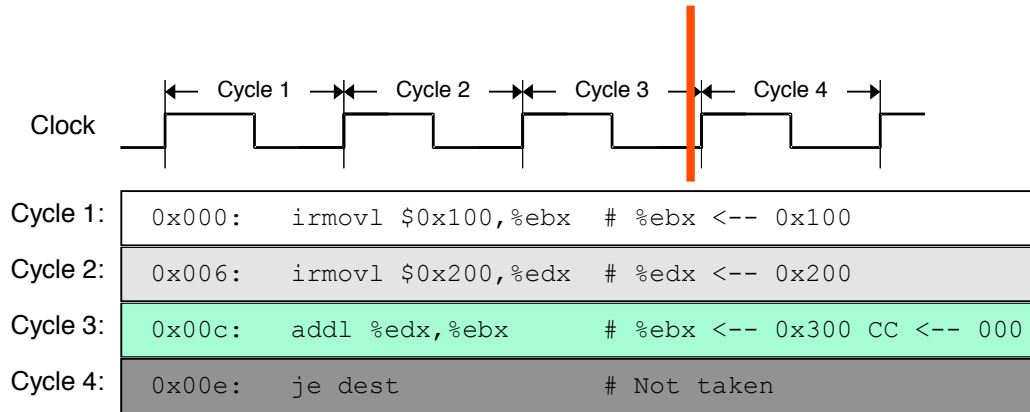



- state set according to second `irmovl` instruction
- combinational logic generates results for `addl` instruction

# SEQ Operation #4

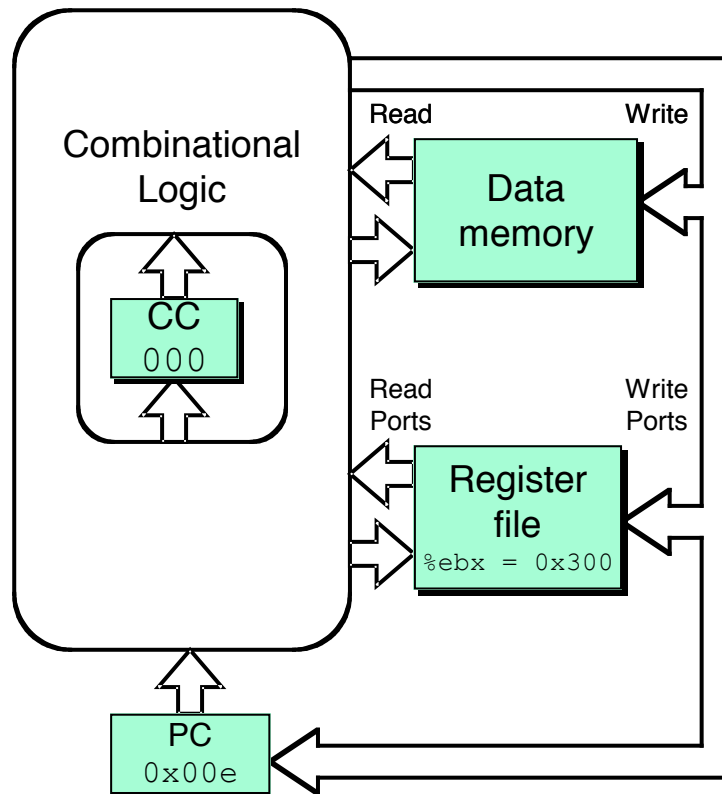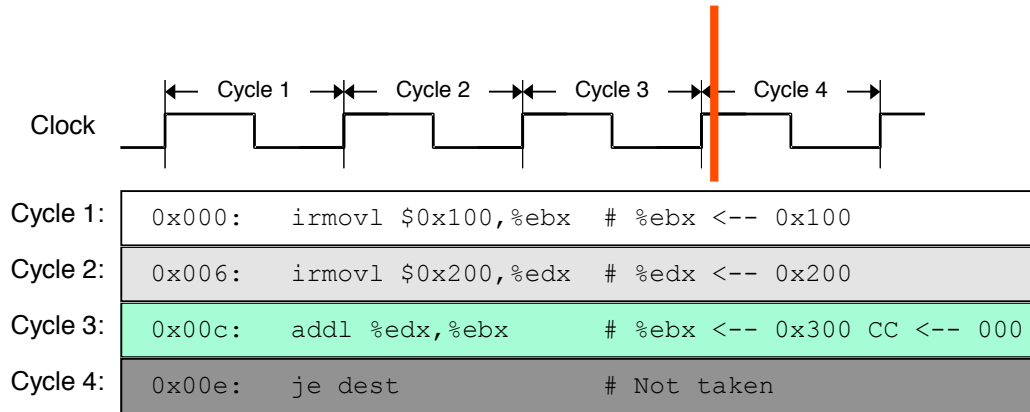

- state set according to addl instruction
- combinational logic starting to react to state changes

# SEQ Operation #5

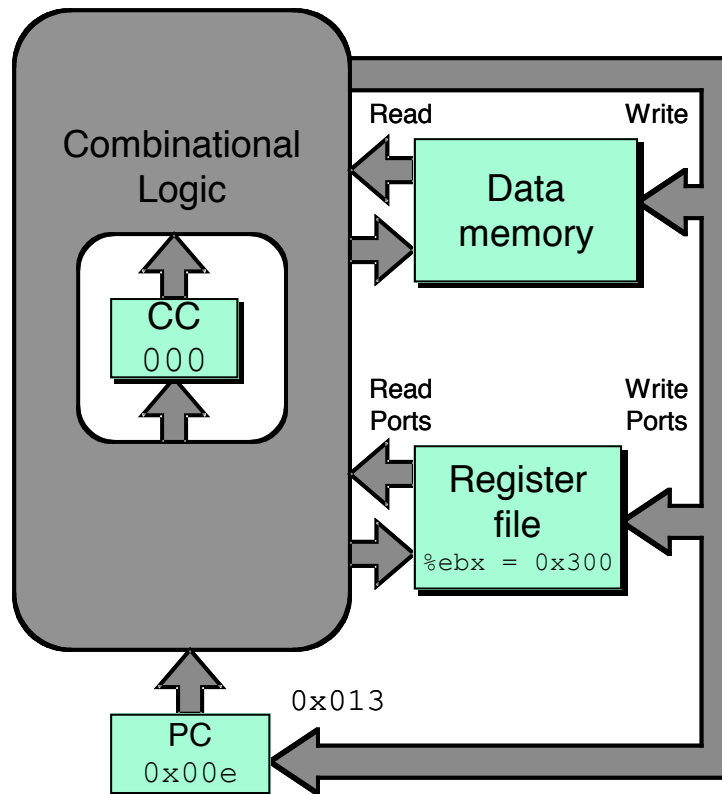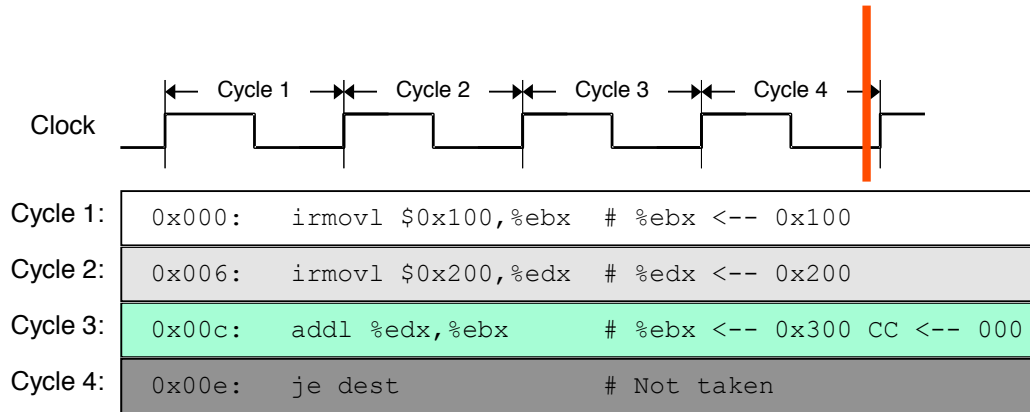

- state set according to addl instruction
- combinational logic generates results for je instruction

# SEQ Summary

## Implementation

- Express every instruction as series of simple steps
- Follow same general flow for each instruction type
- Assemble registers, memories, predesigned combinational blocks
- Connect with control logic

## Limitations

- Too slow to be practical
- In one cycle, must propagate through instruction memory, register file, ALU, and data memory
- Would need to run clock very slowly
- Hardware units only active for fraction of clock cycle