

Systems I

Logic Design I

Topics

- Digital logic
- Logic gates
- Simple combinational logic circuits

A Simple C statement.....

C = A + B;

What pieces of hardware do you think you might need?

- **Storage - for values A, B, C**
- **Computation logic - to compute +**
- **A way to tell the computer to retrieve the values from storage, add them together, and put the result back in storage**
 - **This could be accomplished with a single command (instruction) or with multiple of them.**

Overview of Logic Design


Fundamental Hardware Requirements

- **Communication**
 - How to get values from one place to another
- **Computation**
- **Storage**

Bits are Our Friends


- **Everything expressed in terms of values 0 and 1**
- **Communication**
 - Low or high voltage on wire
- **Computation**
 - Compute Boolean functions
- **Storage**
 - Store bits of information

Digital Signals

 


- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small, and fast

Computing with Logic Gates

 


 - Logic gates constructed from transistors
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
 - With some, small delay



Truth Tables


And

 

$$\text{out} = a \ \&\& \ b$$

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1


Or

 

$$\text{out} = a \ || \ b$$

a	b	out
0	0	0
0	1	1
1	0	1
1	1	1


Not

 

$$\text{out} = !a$$

a	out
0	1
1	0

What about this?

 


out = !((a && b) || c)

out = ~(a*b + c)

a	b	c	out
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


Combinational Circuits

 

Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

Bit Equality

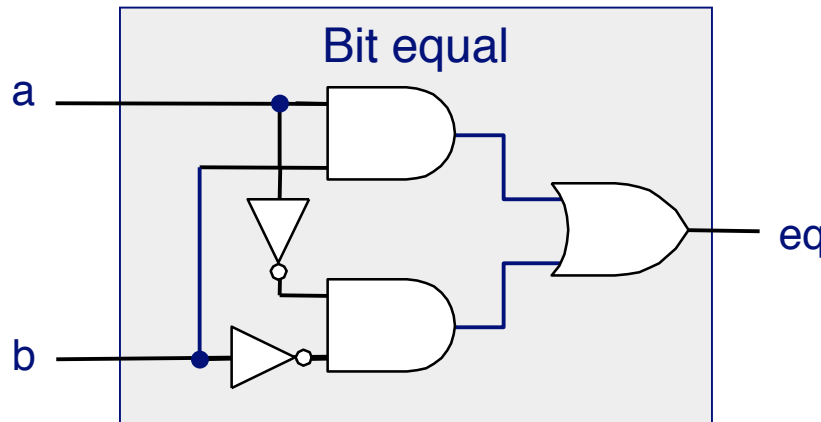

HCL Expression

```
bool eq = (a&&b) || (!a&&!b)
```

- Generate 1 if a and b are equal

Hardware Control Language (HCL)

- Very simple hardware description language
 - Boolean operations have syntax similar to C logical operations
- We'll use it to describe control logic for processors

Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
 - Parts we want to explore and modify

Data Types

- `bool`: Boolean
 - `a, b, c, ...`
- `int`: words
 - `A, B, C, ...`
 - Does not specify word size---bytes, 32-bit words, ...

Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

HCL Operations

- Classify by type of value returned

Boolean Expressions

- Logic Operations

- `a && b, a || b, !a`

- Word Comparisons

- `A == B, A != B, A < B, A <= B, A >= B, A > B`

- Set Membership

- `A in { B, C, D }`

- » Same as `A == B || A == C || A == D`

Word Expressions


- Case expressions

- `[a : A; b : B; c : C]`


- Evaluate test expressions `a, b, c, ...` in sequence

- Return word expression `A, B, C, ...` for first successful test

Word Equality

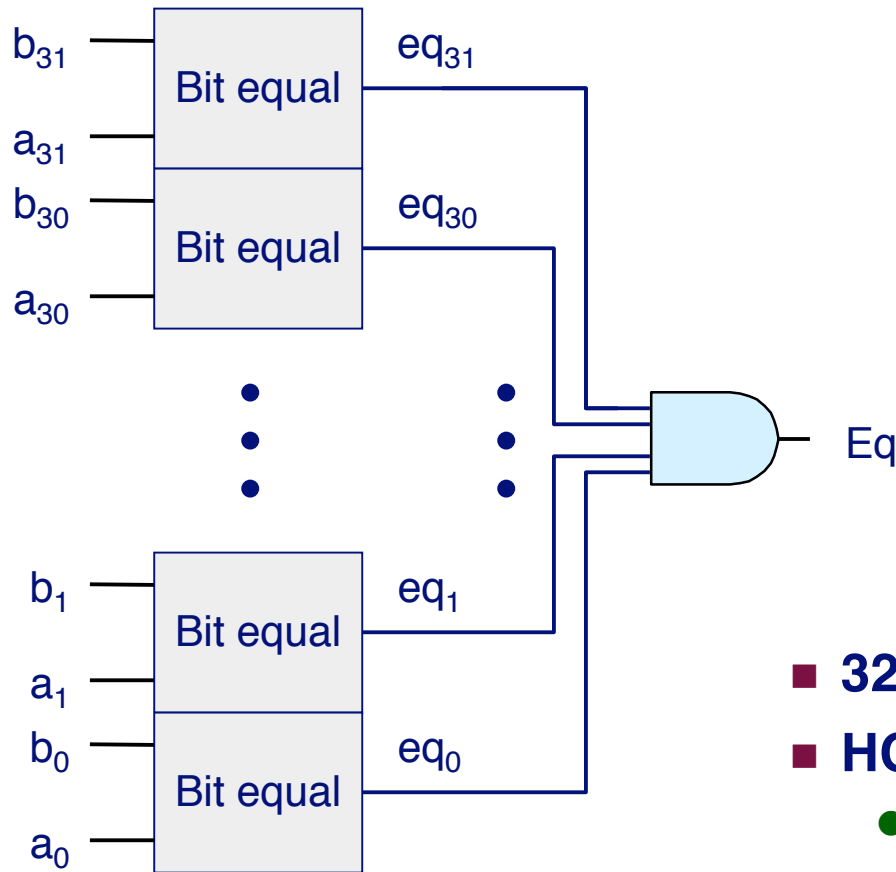

Word-Level Representation

 


HCL Representation

```
bool Eq = (A == B)
```

- 32-bit word size
- HCL representation
 - Equality operation
 - Generates Boolean value

Bit-Level Multiplexor

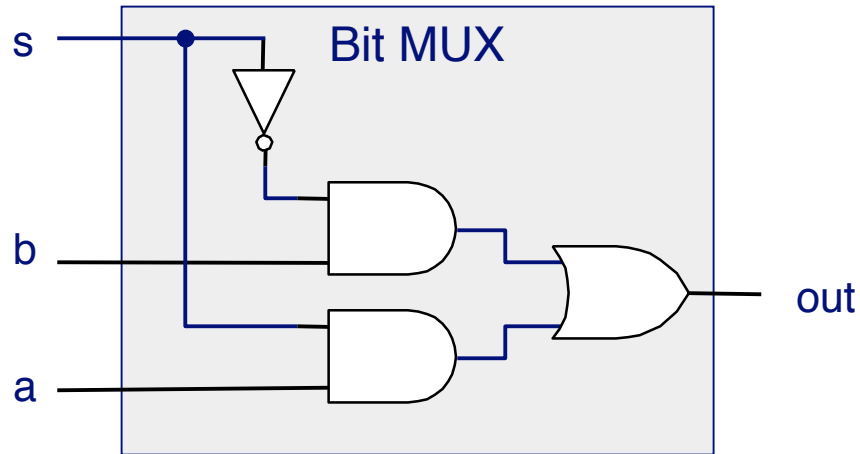


HCL Expression


```
bool out = (s&&a) || (!s&&b)
```

- Control signal **s**
- Data signals **a** and **b**
- Output **a** when **s=1**, **b** when **s=0**

Word Multiplexor

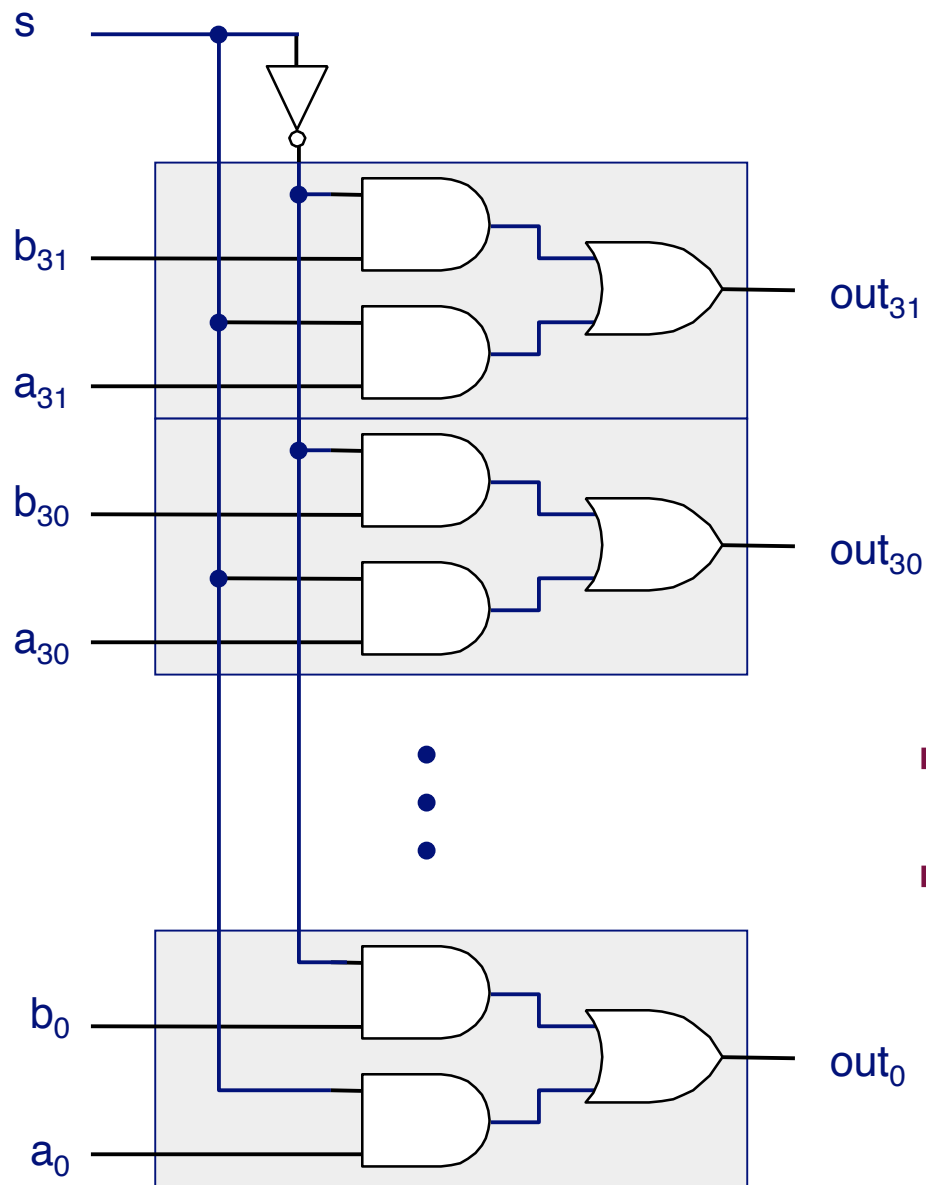

Word-Level Representation

 


HCL Representation

```
int Out = [  
    s : A;  
    1 : B;  
];
```

- Select input word A or B depending on control signal s
- HCL representation
 - Case expression
 - Series of test : value pairs
 - Output value for first successful test

HCL Word-Level Examples


Minimum of 3 Words

 

```
int Min3 = [  
    A < B && A < C : A;  
    B < A && B < C : B;  
    1                : C;  
];
```

- Find minimum of three input words
- HCL case expression
- Final case guarantees match
- How would you build this?

4-Way Multiplexor

 


```
int Out4 = [  
    !s1&&!s0: D0;  
    !s1      : D1;  
    !s0      : D2;  
    1        : D3;  
];
```

- Select one of 4 inputs based on two control bits
- HCL case expression
- Simplify tests by assuming sequential matching

Simple computations are just combinational logic circuits

One Bit Adder

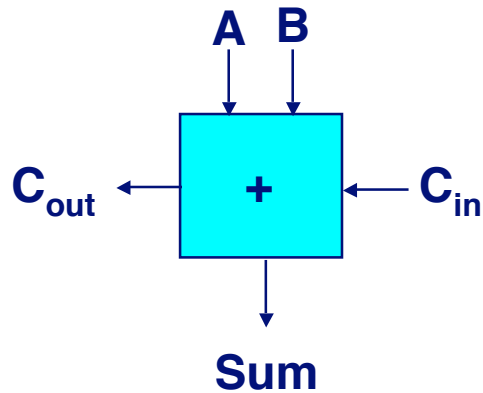


$$\text{Sum} = A \cdot B + A \cdot C_{in} + B \cdot C_{in}$$

$$\begin{aligned} C_{out} &= A \wedge B \wedge C_{in} \\ &= A \cdot B \cdot C_{in} + A \cdot B \cdot C_{in} + A \cdot B \cdot C_{in} + A \cdot B \cdot C_{in} \end{aligned}$$


How do you do subtract?

Four Bit Adder

 


How do you do multiply?

Arithmetic Logic Unit

 

- **Combinational logic**
 - Continuously responding to inputs
- **Control signal selects function computed**
 - Corresponding to 4 arithmetic/logical operations in Y86
- **Also computes values for condition codes**
 - OF = overflow flag, ZF = Zero Flag, SF = Sign Flag

Arithmetic Logic Unit

 

```
int Out = [  
    !s1&&!s0: X+Y;  
    !s1&& s0: Y-Y;  
    s1&&!s0: X&Y;  
    1       : X^Y;  
];
```

Summary

Today

- Basic logic elements
- Combinational logic circuits
 - Truth tables, gates
- Aggregating logic elements
 - Multiplexors, ALUs, etc.

Next Time

- Circuits that remember