




# Combinational Logic





# Multi-input gates - $(x+(y*z))'$

<i>x</i>	<i>y</i>	<i>z</i>	<i>out</i>
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 


Very easy with inverting gates


 
# Half Adder

- 1-bit addition ( $x + y$ )
  - outputs: sum  $s$  and carry  $c$
  - $s = xy' + x'y$  ( $x$  XOR  $y$  or  $x \oplus y$ )
  - $c = xy$



$x$	$y$	$s$	$c$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1




# Full 1-bit adder

- Need a carry in  $c_i$

$$\begin{aligned} s &= x'y c_i' + x y' c_i' + x'y' c_i + x y c_i \\ &= c_i' (x'y + x y') + c_i (x y + x'y') \\ &= c_i' (x'y + x y') + c_i (x'y + x y')' \\ &= c_i \oplus (x \oplus y) \end{aligned}$$
 
$$\begin{aligned} c_o &= x'y c_i + x y' c_i + x y c_i' + x y c_i \\ &= c_i (x'y + x y') + x y (c_i' + c_i) \\ &= c_i (x \oplus y) + x y \end{aligned}$$




$x$	$y$	$c_i$	$s$	$c_o$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



 
# CMOS adder

For the carry, we can first use De Morgan's laws



 
For the **xor**, recall that  $a \text{ xor } b = ab' + a'b$  and  $(a \text{ xor } b)' = ab + a'b'$





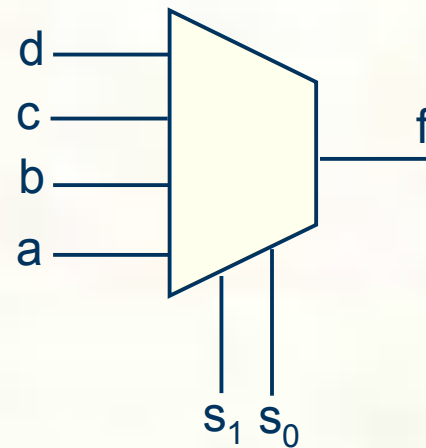
# Multiplexor

- A multiplexor (selector or mux) selects one of  $n$  inputs to be output



- Let's make it easy and start with a 2-input mux

 - when  $s = 0$ ,  $f = a$
- when  $s = 1$ ,  $f = b$






# 2 input Multiplexor design

<i>s</i>	<i>a</i>	<i>b</i>	<i>f</i>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 
$$\begin{aligned} f &= s'ab' + s'ab + sa'b + sab \\ &= s'a(b'+b) + sb(a'+a) \\ &= s'a + sb \end{aligned}$$




 
# Making bigger muxes

You can design them directly, or just glue together smaller muxes:








 
# Decoders

- Decode an  $n$ -bit input to set output line  $2^n - 1$



$a$	$b$	$00$	$01$	$10$	$11$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 



# Programmable Logic Array (PLA)

- Since all Boolean functions can be expressed in sum of products form, we can implement a set of  $n$  input functions systematically in hardware using a PLA

