

Lecture 11: A Simple Datapath & Pipelining

- Last time
 - Exam discussion (average 73 before regrade)
 - Broke down execution & state (IF, ID, EX, MEM, WB)
 - PC state
 - By instruction type: Control, Register, Memory
- Today
 - Take QUIZ 7 over P&H 4.5-6, before 11:59pm today
 - Homework 4 due Thursday March 4
 - Putting the parts together
 - Logic & control
 - How can we execute instructions faster?
 - multicycle execution
 - pipelining


UTCS 352, Lecture 11

1

5 Stages for Multicycle Execution

5 logical and distinct steps

 IF: fetch instruction
ID/R: decode instruction
and read registers
EX: execute (add, sub, ...)
MEM: access memory
WB: store result (write back)




UTCS 352, Lecture 11

2

What do we need to execute instructions?


Which instruction?

- instruction memory, PC: `beq, j`

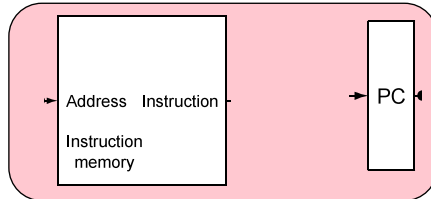

Which registers?


- register storage file

 

Which Math?

- combinational logic:


`add, sub,`
`and, or, slt`

 

Which data?

- memory:

`lw, sw`

 

UTCS 352, Lecture 11

3


Creating a Datapath from the Parts

- Assemble the datapath segments, add control lines, and multiplexors
- **Single cycle** design - fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - **multiplexors (mux)** needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the Register File and Data Memory
- Cycle time is determined by length of the longest path

UTCS 352, Lecture 11

4

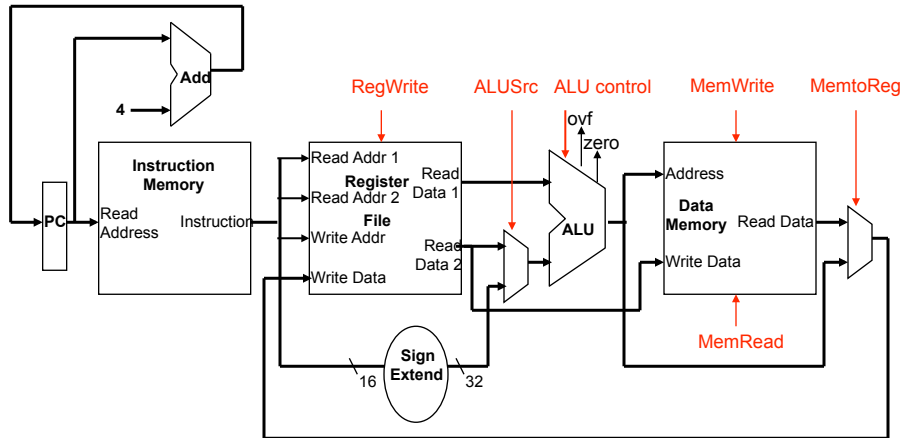
Simplified Datapath Fetch, R, and Memory Access Portions



UTCS 352, Lecture 11

5

More Datapath with Multiplexors


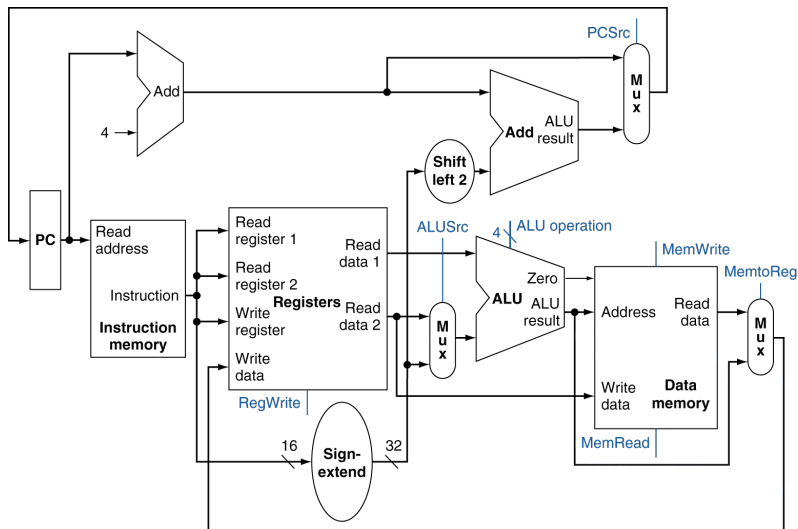


UTCS 352, Lecture 11

6

How do we convert instruction bits to ALU control bits?

Example: add \$8, \$17, \$18

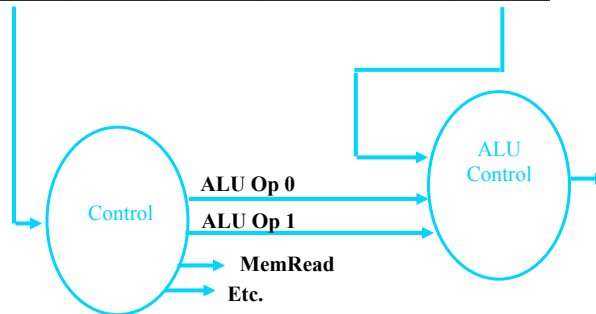 


0000 AND
 0001 OR
 0010 add
 0110 subtract
 0111 set-on-less-than
 1100 NOR

UTCS 352, Lecture 11

9

ALU Active on All Instructions

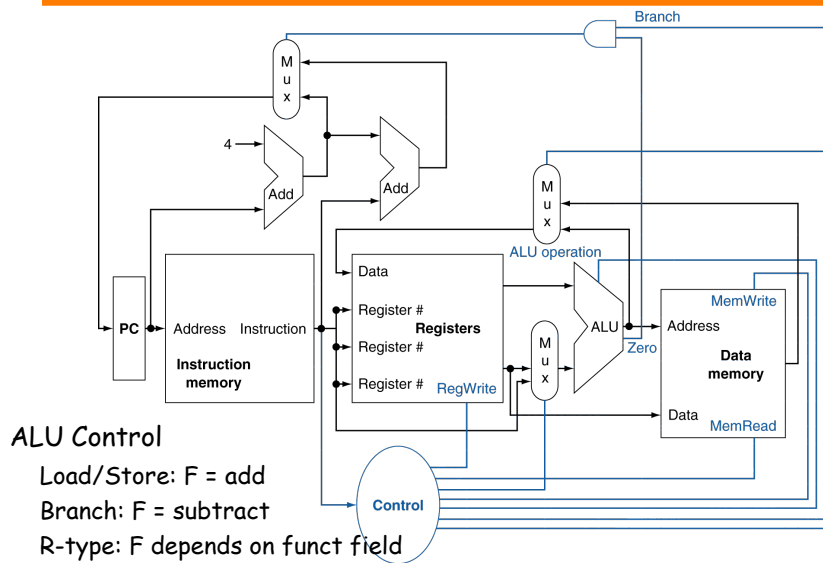

10

ALU Control


2-bit ALUOp **derived** from opcode

- Combinational logic derives ALU control


4-bit ALU control **derived** from opcode

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111


Datapath With Control

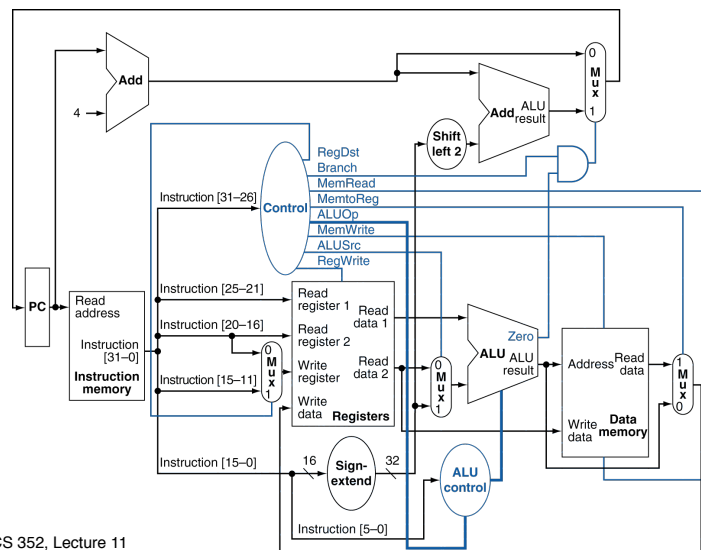

R-Type Instruction

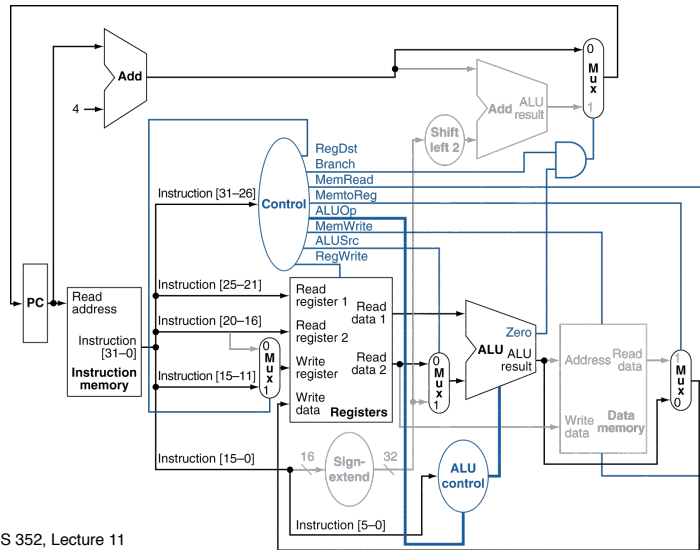

Datapath With Jumps Added

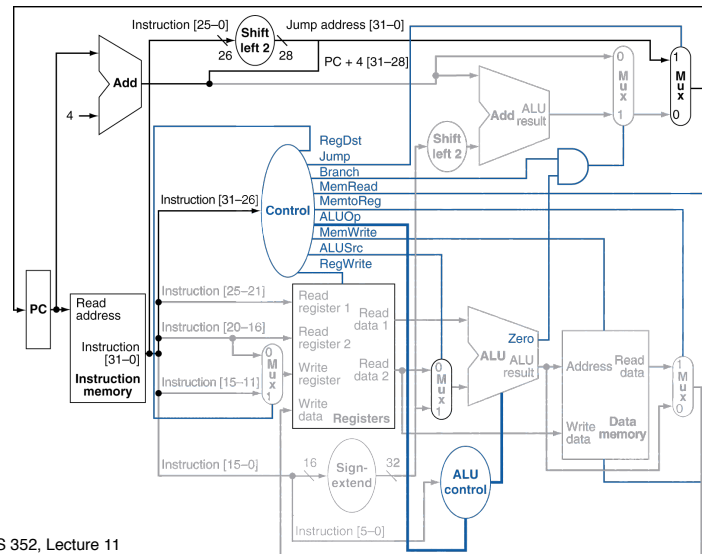


Performance Issues


- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period based on instruction
- Violates design principle
 - Making the common case fast
- **Motivates multiple (5) steps**

Single Cycle vs. Multiple Cycle Timing


Single Cycle Implementation:

 

Multiple Cycle Implementation:

 

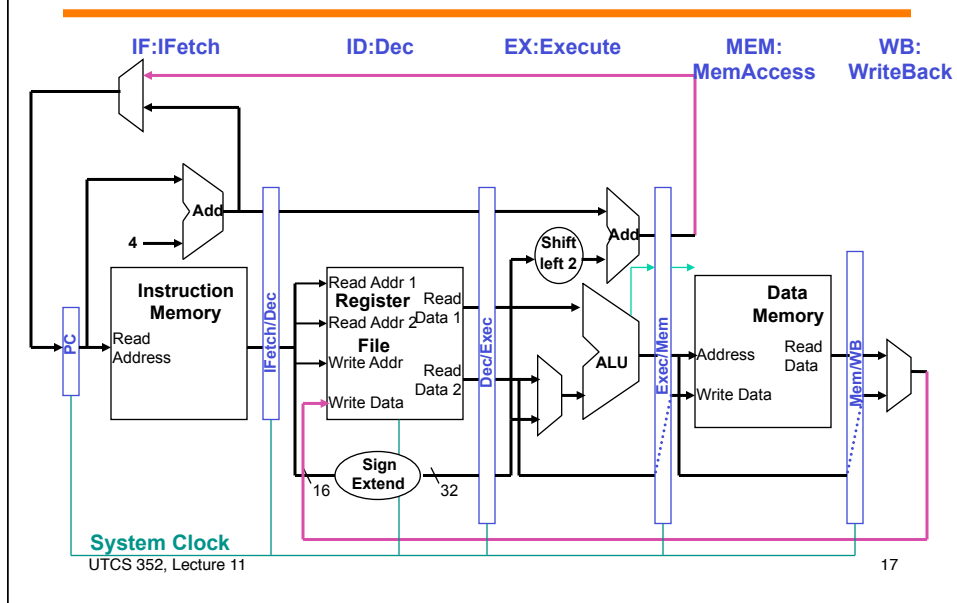MIPS Multicycle Datapath logical division of states



How Can We Make it Faster?

- Split the multiple instruction cycle into smaller and smaller steps
 - Point of diminishing returns where as much time is spent loading the state registers as doing the work
- Start fetching and executing the next instruction before the current one has completed
 - **Pipelining** - (all?) modern processors are pipelined for performance
 - Remember *the* performance equation:

$$\text{CPU time} = \text{IC} * \text{CPI} * \text{CCT}$$
- Fetch & execute more than one instruction at a time!
 - Superscalar processing - stay tuned


Pipelining is Natural!

Laundry Example


- Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Dryer takes 30 minutes
- "Folder" takes 30 minutes
- "Stasher" takes 30 minutes to put clothes into drawers



Sequential Laundry

 

Pipelined Laundry: Start work ASAP

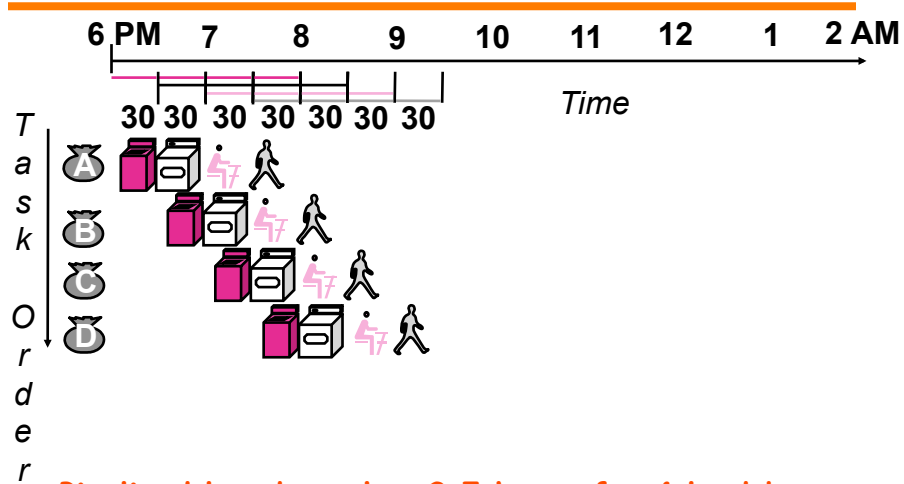


- Pipelined laundry takes 3.5 hours for 4 loads!

UTCS 352, Lecture 11

21

Pipelining Lessons

 


- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup
- Time to "**fill**" pipeline and time to "**drain**" it reduces speedup
- Stall for Dependences

UTCS 352, Lecture 11

22

A Pipelined MIPS Processor

 
- Start the **next** instruction before the current one has completed
 - improves **throughput** - total amount of work done in a given time
 - instruction **latency** (execution time, delay time, response time - time from the start of an instruction to its completion) is *not* reduced




- clock cycle (pipeline stage time) is limited by the slowest stage
- for some instructions, some stages are **wasted** cycles

Single Cycle, Multiple Cycle, vs. Pipeline


Single Cycle Implementation:

 

Multiple Cycle Implementation:

 


Pipeline Implementation:

 

MIPS Pipeline Datapath Modifications

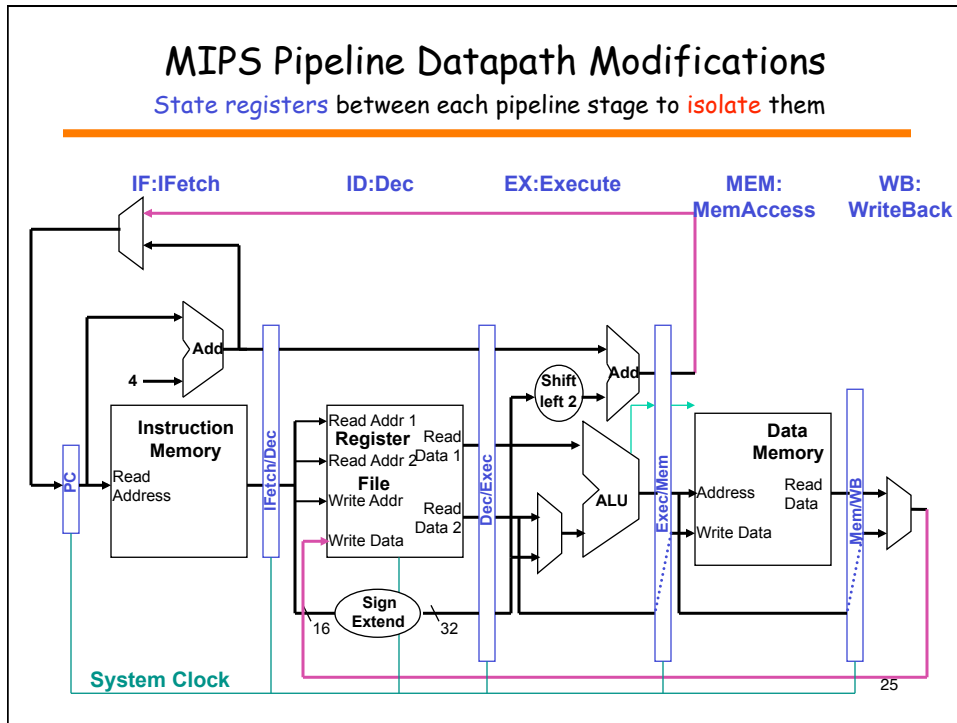State registers between each pipeline stage to isolate them



Pipelining the MIPS ISA

- What makes it easy
 - all instructions are the same length (32 bits)
 - can fetch in the 1st stage and decode in the 2nd stage
 - few instruction formats (three) with **symmetry** across formats
 - can begin reading register file in 2nd stage
 - memory operations can occur only in loads and stores
 - can use the execute stage to calculate memory addresses
 - each MIPS instruction writes at most one result (i.e., changes the machine state) and does so near the end of the pipeline (MEM and WB)
- What makes it hard
 - **structural hazards**: what if we had only one memory?
 - **control hazards**: what about branches?
 - **data hazards**: what if an instruction's input operands depend on the output of a previous instruction?

How Much Performance?

- If all stages are balanced (all take the same time)
- Ideal Speedup = Instructions/Number of Stages
- Why it is never ideal:
 - Stages are never perfectly balanced
 - Pipeline fill and drain
 - Breaking down of instructions into stages adds time to each stage:
 - Time between stages_{pipelined} > Time between instructions_{nonpipelined}
- Speedup due to increased throughput
 - Latency (time for each instruction) does not decrease

Summary

- Simplistic version of pipelining
 - Pipelining improves instruction throughput
 - Longest stage determines latency
- Next Time
 - Realistic version of Pipelining
 - Hazards & forwarding
 - Homework 4 is due Thursday March 4, 2010
- Reading: P&H 4.7-10